

# Cell Library Databook

by Team S5

H. Lovett (hl13g10)

A. J. Robinson (ajr2g10)

C. Schepens (cs7g10)

M. Wearn (mw20g10)

December 9, 2013

## Contents

1	And2	4
2	buffer	5
3	fulladder	6
4	halfadder	7
5	Inverter	8
6	leftbuf	9
7	mux2	10
8	nand2	11
9	nand3	12
10	nand4	13
11	nor2	14
12	nor3	15
13	or2	16
14	rightend	17
15	rowcrosser	18
16	scandtype	19
17	scanreg	20
18	tiehigh	21
19	tielow	22
20	trisbuf	23
21	xor2	24
A	Appendix A	25
A.1	Team Management . . . . .	25
A.2	Division of Labour . . . . .	26


<b>B</b>	<b>Design Detail</b>	<b>27</b>
B.1	fulladder . . . . .	28
B.2	halfadder . . . . .	30
B.3	leftbuf . . . . .	31
B.4	rdtype . . . . .	32
B.5	smux2 . . . . .	34
B.6	smux3 . . . . .	36
B.7	xor2 . . . . .	38

# 1 And2


**Designer:** Constantijn Schepens

**Cell Description:** A two input AND gate

Symbol

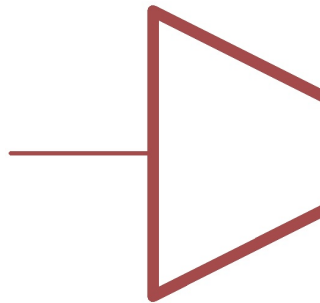

Circuit Diagram

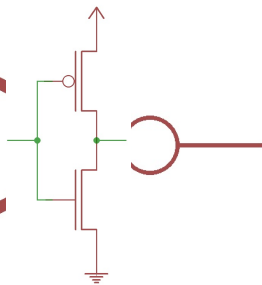


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

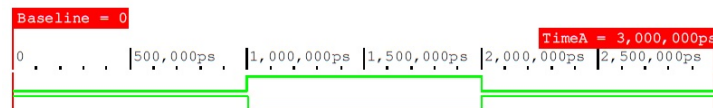


## 2 buffer


**Designer:** Ashley Robinson

**Cell Description:** A non-inverting buffer

**Symbol**

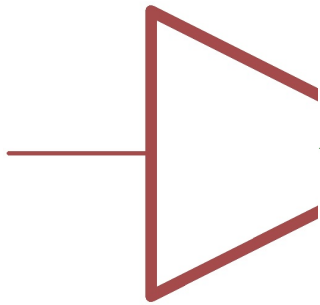

**Circuit Diagram**

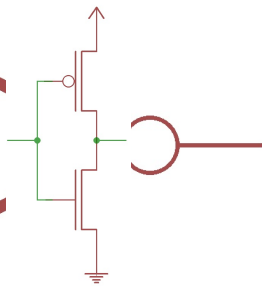


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
A to Y	134.2

**System Verilog Simulation**

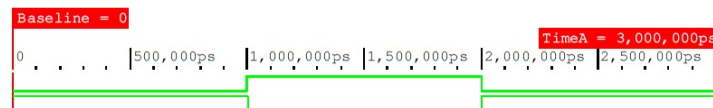


### 3 fulladder

**Designer:** Martin Wearn

**Cell Description:** Adds two bit values and the previous bitscie carry out, to produce a sum and carry


**Symbol**

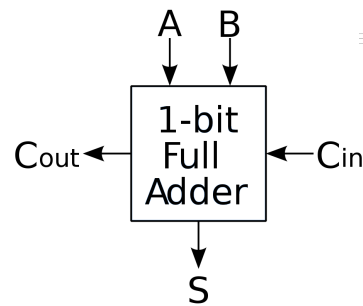

**Circuit Diagram**




**Dimensions**

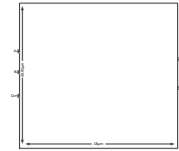

**AC Characteristics**

A to S/Cout prop delay (tPA) 331.7ps B to S/Cout prop delay (tPB) 358.3ps Cin to S/Cout prop delay (tP

**System Verilog Simulation**

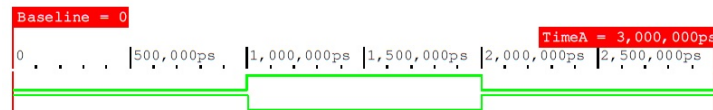


## 4 halfadder

**Designer:** Martin Wearn


**Cell Description:** Adds two bits to produce a sum and carry

**Symbol**

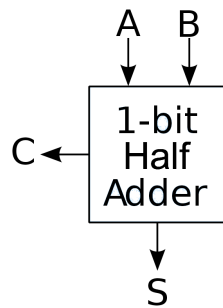

**Circuit Diagram**


**Dimensions**

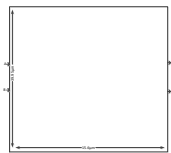

**AC Characteristics**

Signal		Delay (ps)
A to S/Cout prop delay (tPA)	256.2ps	B to S/Cout prop delay (tPB) 242.8ps

**System Verilog Simulation**

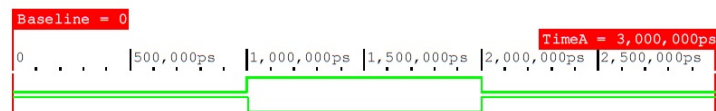


## 5 Inverter


**Designer:** Henry Lovett

**Cell Description:** A basic inverter gate

### Symbol

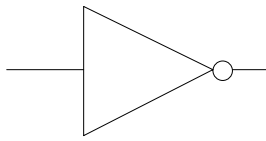


### Dimensions

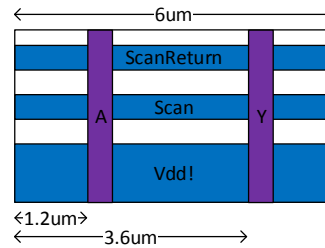

### AC Characteristics

Signal	Delay (ps)
TO BE	DONE

### System Verilog Simulation

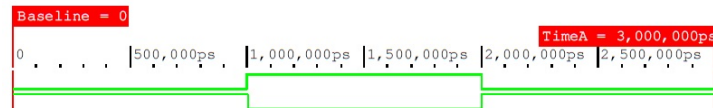




## 6 leftbuf

**Designer:** Henry Lovett


**Cell Description:** A start of row buffer cell.

**Symbol**

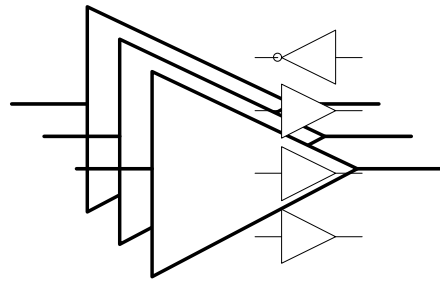

**Circuit Diagram**


**Dimensions**

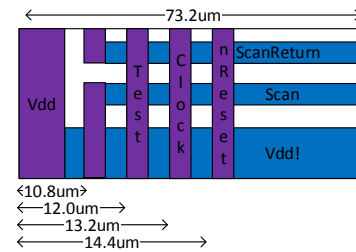

**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

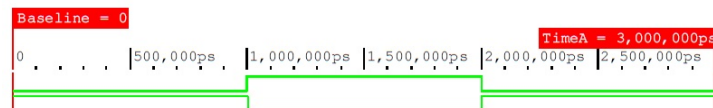


## 7 mux2


**Designer:** Constantijn Schepens

**Cell Description:** A two input Multiplexor

**Symbol**

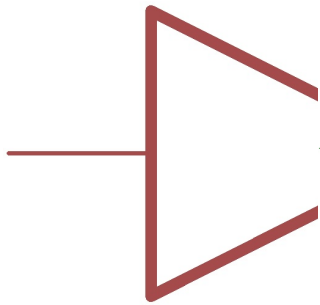

**Circuit Diagram**

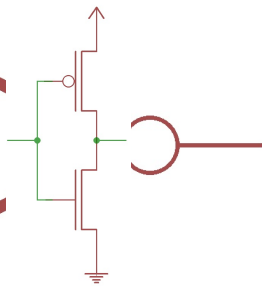


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

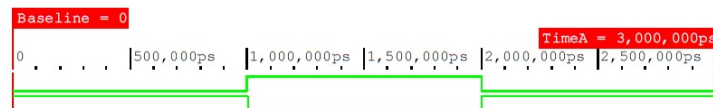


## 8 nand2


**Designer:** Constantijn Schepens

**Cell Description:** A two input NAND gate

**Symbol**

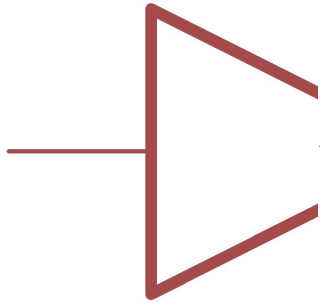

**Circuit Diagram**

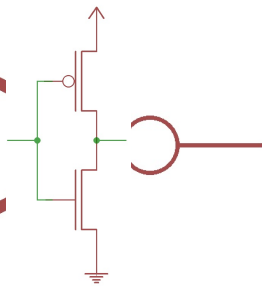


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

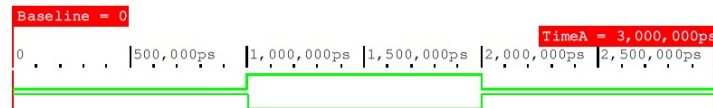


## 9 nand3


**Designer:** Constantijn Schepens

**Cell Description:** A two input NAND gate

Symbol

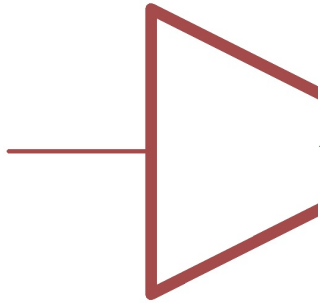

Circuit Diagram

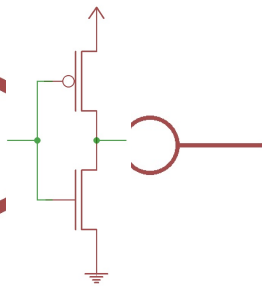


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

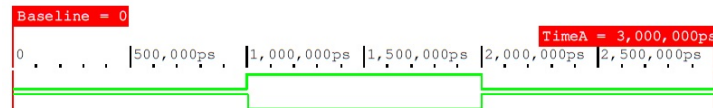


## 10 nand4


**Designer:** Constantijn Schepens

**Cell Description:** A two input NAND gate

**Symbol**

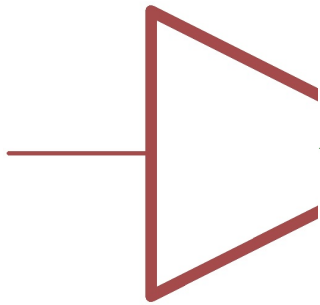

**Circuit Diagram**

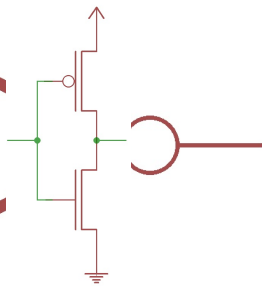


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

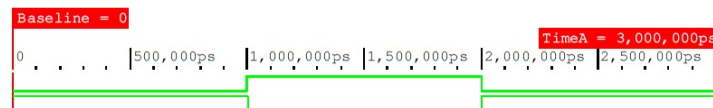


## 11 nor2


**Designer:** Henry Lovett

**Cell Description:** A two input NOR gate

### Symbol

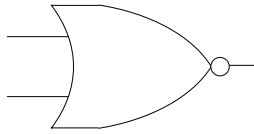


### Dimensions

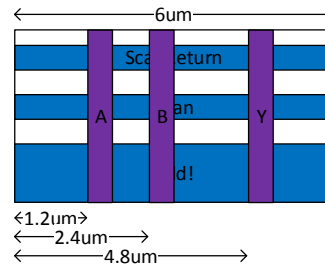

### AC Characteristics

Signal	Delay (ps)
TO BE	DONE

### System Verilog Simulation

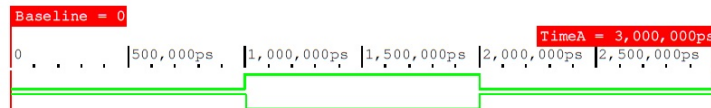


## 12 nor3


**Designer:** Henry Lovett

**Cell Description:** A three input NOR gate

### Symbol

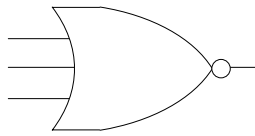


### Dimensions

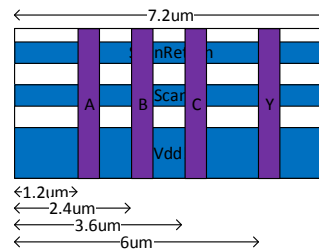

### AC Characteristics

Signal	Delay (ps)
TO BE	DONE

### System Verilog Simulation

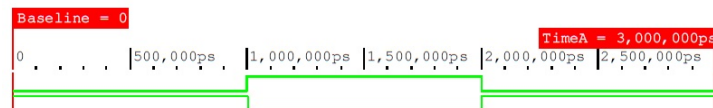


## 13 or2


**Designer:** Henry Lovett

**Cell Description:** A two input OR gate

### Symbol

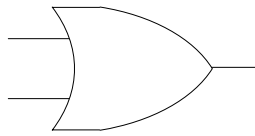


### Dimensions

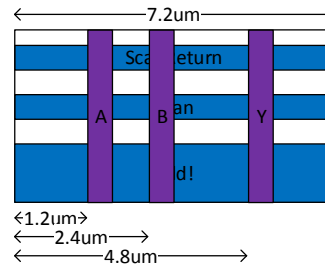

### AC Characteristics

Signal	Delay (ps)
TO BE	DONE

### System Verilog Simulation

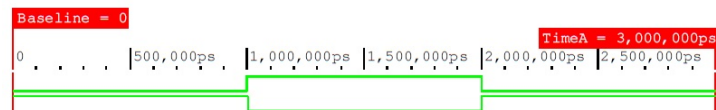





14 rightend

**Designer:** Henry Lovett  
**Cell Description:** An end of row buffer cell.

Symbol

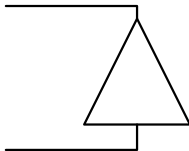


Dimensions

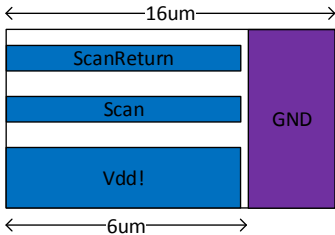

AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

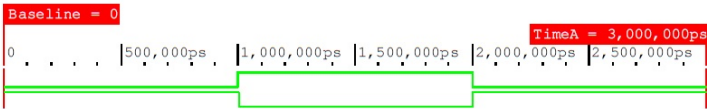


## 15 scandtype


**Designer:** Constantijn Schepens

**Cell Description:** A Raw DType cell

**Symbol**

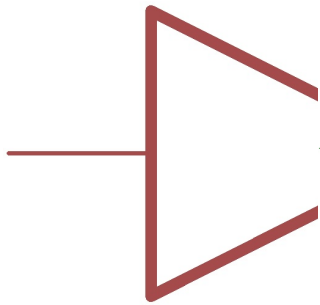

**Circuit Diagram**

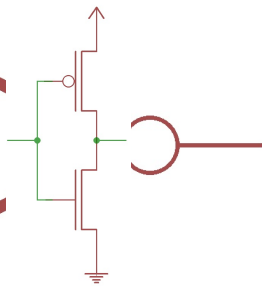


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

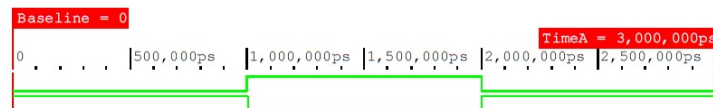


## 16 scanreg


**Designer:** Constantijn Schepens

**Cell Description:** A Raw DType cell

Symbol

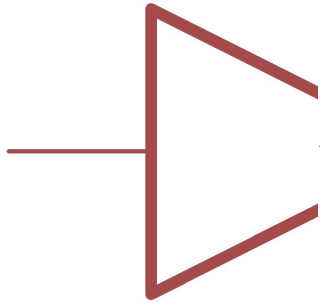

Circuit Diagram

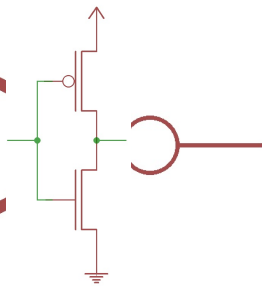


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

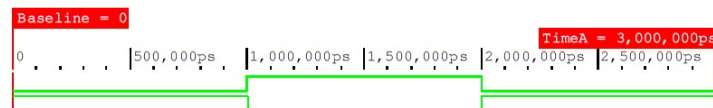


## 17 Rowcrosser

## 18 trisbuf


**Designer:** Ashley Robinson

**Cell Description:** A tristate buffer

**Symbol**

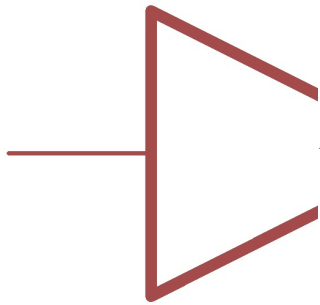

**Circuit Diagram**

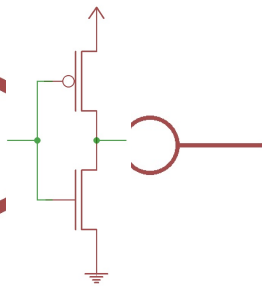


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
TO BE	DONE

**System Verilog Simulation**

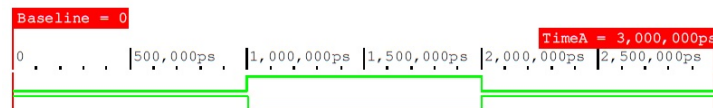


## 19 xor2


**Designer:** Ashley Robinson

**Cell Description:** A two input xor gate

**Symbol**

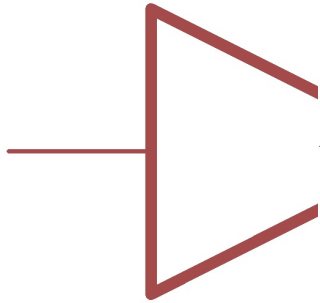

**Circuit Diagram**

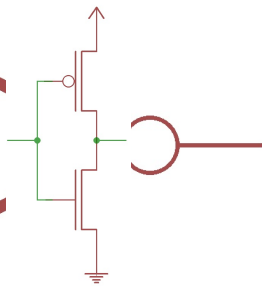


**Dimensions**



**AC Characteristics**

Signal	Delay (ps)
A to Y	273.4
B to Y	193

**System Verilog Simulation**

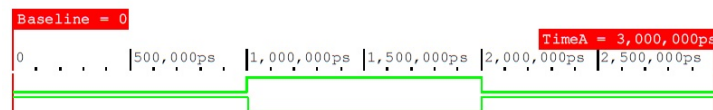

## A Appendix A

### A.1 Team Management

## A.2 Division of Labour

## B Design Detail




## B.1 fulladder

---


**Designer:** Martin Wearn

**Cell Description:** Adds two bit values and the previous bitslice carry out, to produce a sum and carry

### Stick Diagram

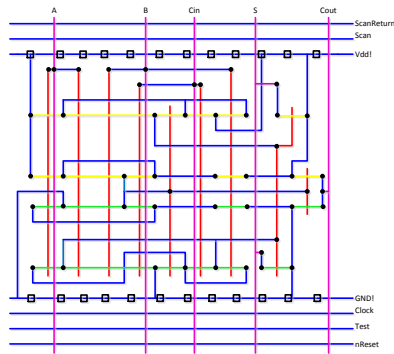

### Transistor Level Circuit Diagram

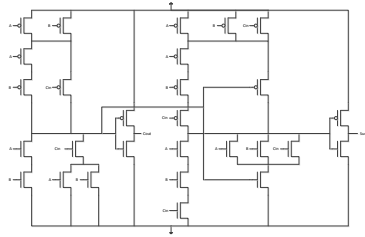


## B.2 halfadder


**Designer:** Martin Wearn

**Cell Description:** Adds two bits to produce a sum and carry

### Stick Diagram

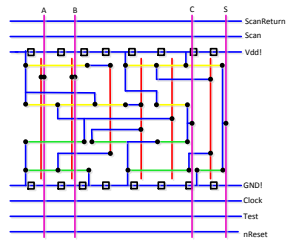

### Transistor Level Circuit Diagram

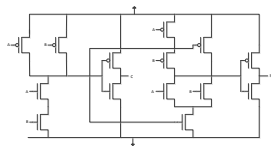


### B.3 leftbuf


**Designer:** Henry Lovett

**Cell Description:** A start of row buffer cell.

#### Stick Diagram

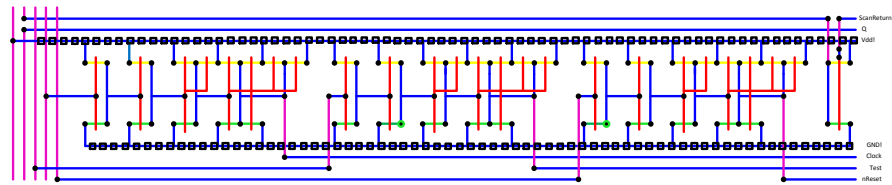

#### Transistor Level Circuit Diagram

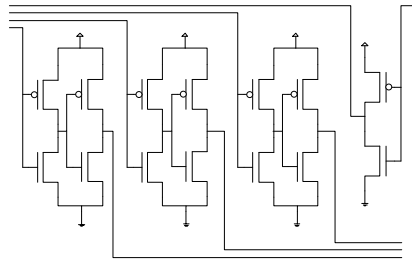


## B.4 rdtype


**Designer:** Ashley Robinson

**Cell Description:** Raw Dtype

### Stick Diagram

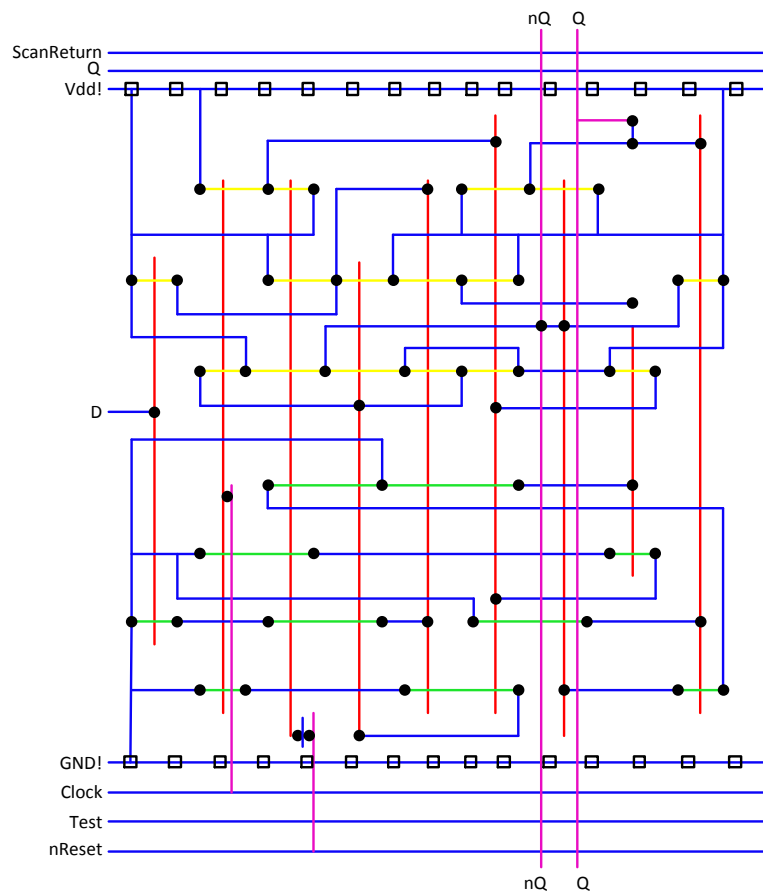

## Transistor Level Circuit Diagram

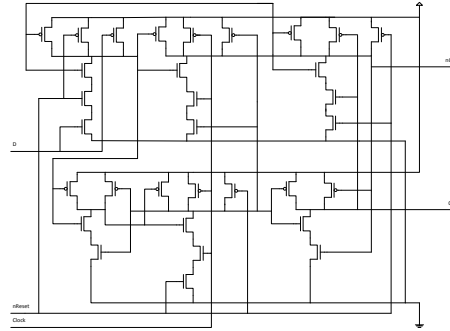


## B.5 smux2

---


**Designer:** Schep

**Cell Description:** A start of row buffer cell.

**Stick Diagram**

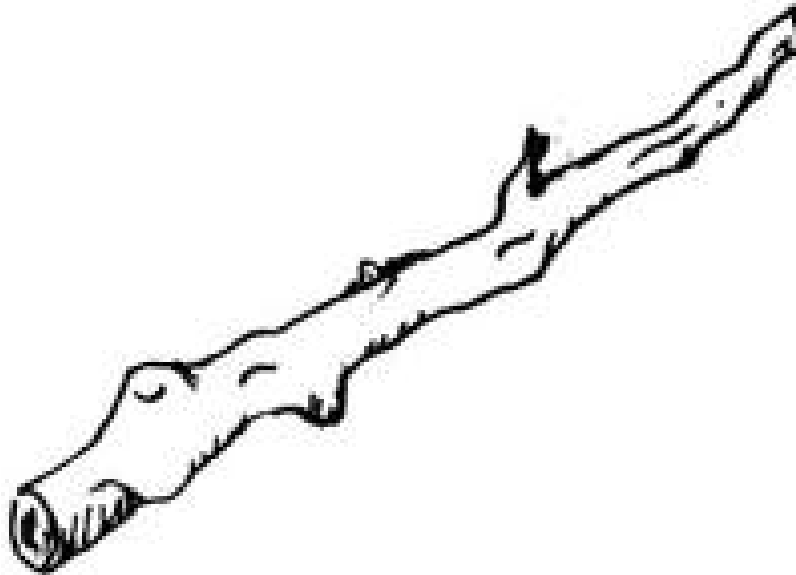

Transistor Level Circuit Diagram

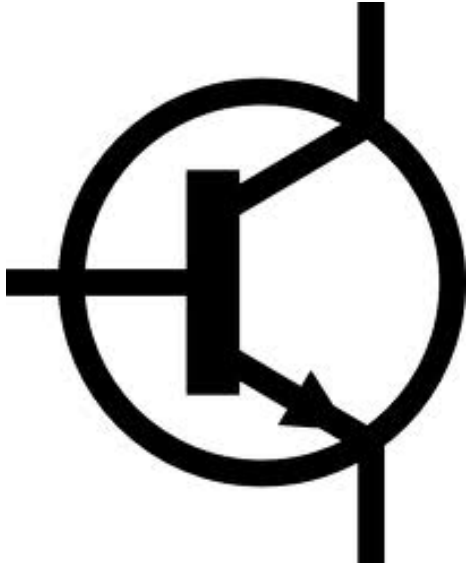




## B.6 smux3

---


**Designer:** Schep

**Cell Description:** A scan multiplexor.

**Stick Diagram**

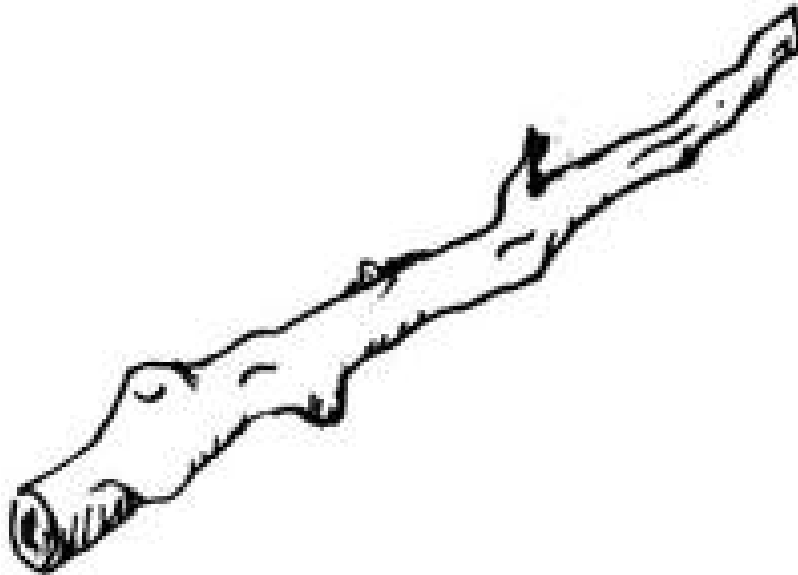

Transistor Level Circuit Diagram

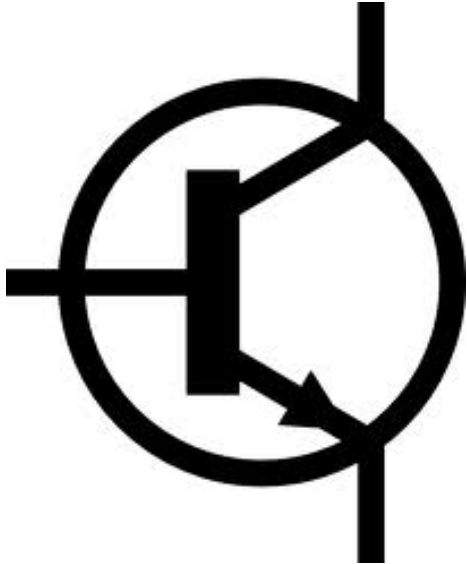


## B.7 xor2

**Designer:** Ashley Robinson

**Cell Description:** A 2 input XOR gate.

### Stick Diagram

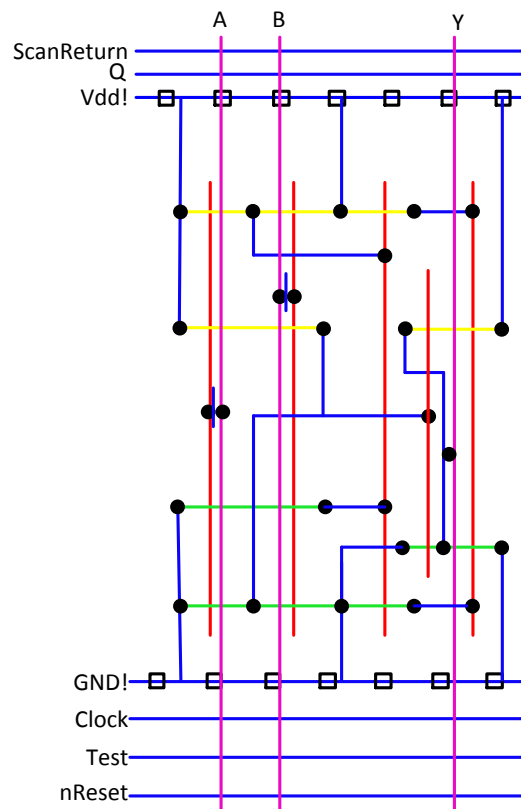

### Transistor Level Circuit Diagram

