

Cell Library Databook

by Team S5

H. Lovett (hl13g10)

A. J. Robinson (ajr2g10)

C. Schepens (cs7g10)

M. Wearn (mw20g10)

December 9, 2013

Contents


1	And2	4
2	buffer	5
3	fulladder	6
4	halfadder	7
5	Inverter	8
6	leftbuf	9
7	mux2	10
8	nand2	11
9	nand3	12
10	nand4	13
11	nor2	14
12	nor3	15
13	or2	16
14	rightend	17
15	scandtype	18
16	scanreg	19
17	Rowcrosser	20
18	Tie High	20
19	Tie Low	20
20	trisbuf	22
21	xor2	23
A	Appendix A	24
A.1	Team Management	24
A.2	Division of Labour	25

B	Design Detail	26
B.1	fulladder	27
B.2	halfadder	29
B.3	leftbuf	30
B.4	rdtype	31
B.5	smux2	33
B.6	smux3	35
B.7	xor2	37


1 And2

Designer: Constantijn Schepens
Cell Description: A two input AND gate


Symbol

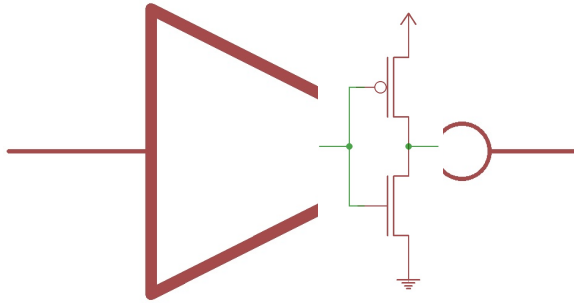

Circuit Diagram

 


Dimensions

 

AC Characteristics

Signal	Delay (ps)
a fall propagation delay	171.4
a rise propagation delay	72.1
b fall propagation delay	179.7
b rise propagation delay	68.3

System Verilog Simulation

 


2 buffer


Designer: Ashley Robinson

Cell Description: A non-inverting buffer

Symbol

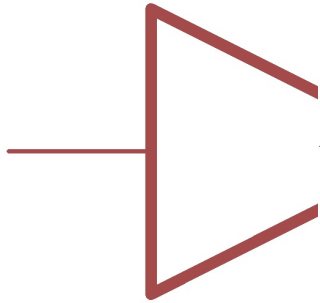

Circuit Diagram

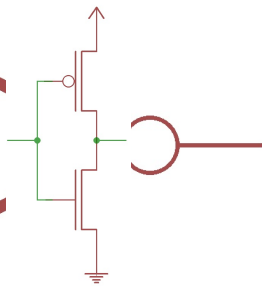


Dimensions



AC Characteristics

Signal	Delay (ps)
prop delay rise	138.5
prop delay fall	129.9
average prop	134.2

System Verilog Simulation

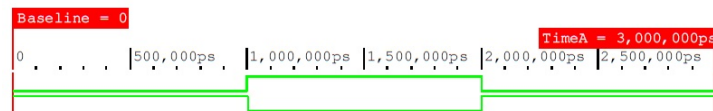


3 fulladder


Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bitslie carry out, to produce a sum and carry


Symbol

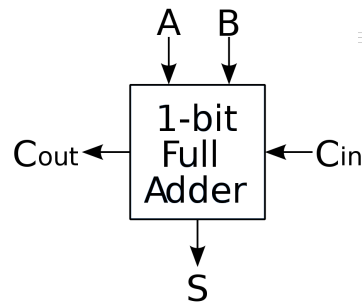

Circuit Diagram

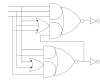


Dimensions

 

AC Characteristics

Signal	Delay (ps)
prop delay as 1	255.7
prop delay bs 1	222.7
prop delay cins 1	208.3
prop delay as 0	334.2
prop delay bs 0	301.9
prop delay cins 0	297.1
prop delay acout 1	262.0
prop delay bcout 1	228.7
prop delay cincout 1	263.5
prop delay acout 0	308.0
prop delay bcout 0	359.3
prop delay cincout 0	285.7

System Verilog Simulation

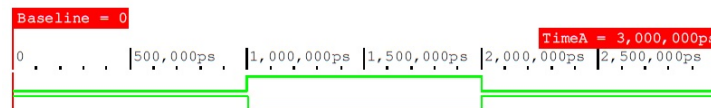


4 halfadder

Designer: Martin Wearn


Cell Description: Adds two bits to produce a sum and carry

Symbol

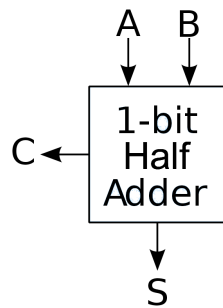

Circuit Diagram


Dimensions

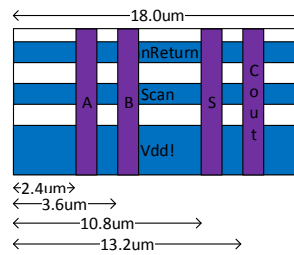

AC Characteristics

Signal	Delay (ps)
prop delay as 1	255.8
prop delay bs 1	244.0
prop delay as 0	247.6
prop delay bs 0	237.8
prop delay ac 1	176.7
prop delay bc 1	184.8
prop delay ac 0	157.4
prop delay bc 0	147.3

System Verilog Simulation

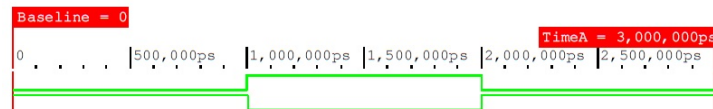


5 Inverter


Designer: Henry Lovett

Cell Description: A basic inverter gate

Symbol

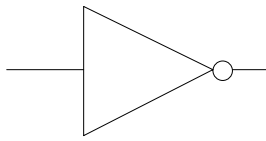


Dimensions

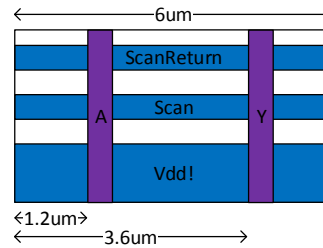

AC Characteristics

Signal	Delay (ps)
a rise delay	107.3
a fall delay	81.7

System Verilog Simulation

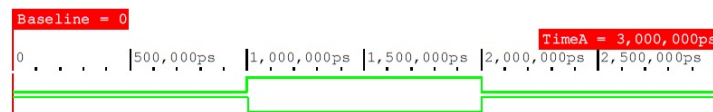

6 leftbuf


Designer: Henry Lovett

Cell Description: A start of row buffer cell.

Symbol

Circuit Diagram


Dimensions

 

AC Characteristics

Signal	Delay (ps)
clock rise prop delay	287.5
clock fall prop delay	271.3
test rise prop delay	282.5
test fall prop delay	272.6
nreset rise prop delay	290.5
nreset fall prop delay	273.2
sdo rise prop delay	124.7
sdo fall prop delay	157.7

System Verilog Simulation

 


7 mux2


Designer: Constantijn Schepens

Cell Description: A two input Multiplexor

Symbol

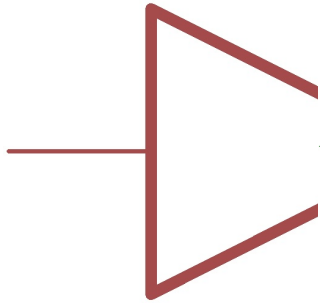

Circuit Diagram

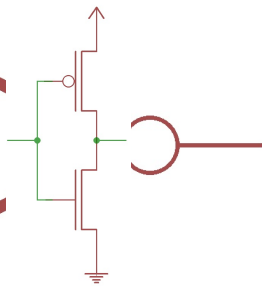


Dimensions



AC Characteristics

Signal	Delay (ps)
i1 rise propagation delay	217.3
i1 fall propagation delay	208.7
i0 rise propagation delay	180.5
i0 fall propagation delay	184.4
s pass i1 rise propagation delay	201.6
s pass i0 fall propagation delay	192.1
s pass i1 fall propagation delay	247.9
s pass i0 rise propagation delay	236.0

System Verilog Simulation

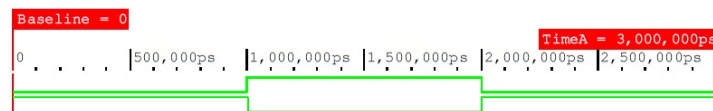


8 nand2

Designer: Constantijn Schepens


Cell Description: A two input NAND gate

Symbol

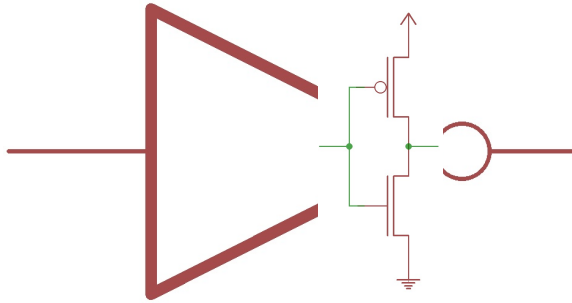

Circuit Diagram


Dimensions

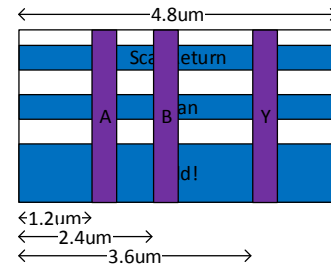

AC Characteristics

Signal	Delay (ps)
a rise propagation delay	118.6
a fall propagation delay	115.5
b rise propagation delay	112.8
b fall propagation delay	122.5

System Verilog Simulation

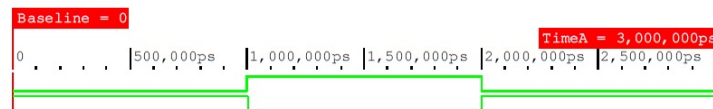


9 nand3


Designer: Constantijn Schepens

Cell Description: A two input NAND gate


Symbol

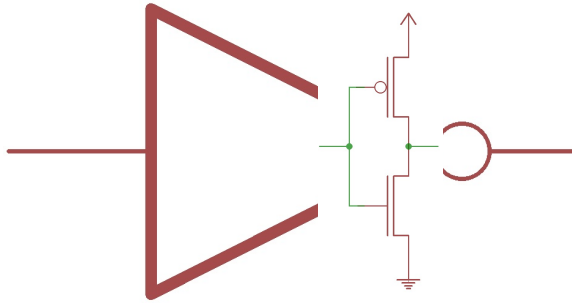

Circuit Diagram

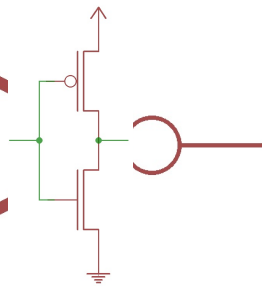


Dimensions

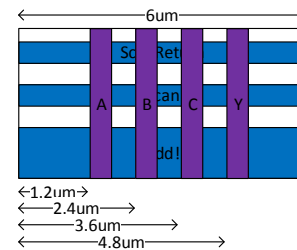

AC Characteristics

Signal	Delay (ps)
a rise propagation delay	128.0
a fall propagation delay	157.6
b rise propagation delay	124.9
b fall propagation delay	159.7
c rise propagation delay	116.7
c fall propagation delay	158.4

System Verilog Simulation

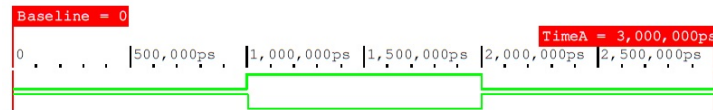


10 nand4


Designer: Constantijn Schepens

Cell Description: A two input NAND gate


Symbol

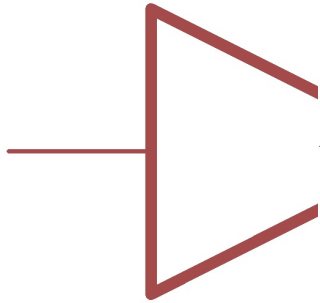

Circuit Diagram

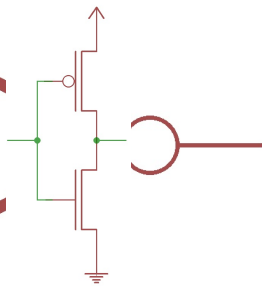


Dimensions

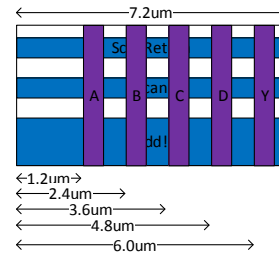

AC Characteristics

Signal	Delay (ps)
a rise propagation delay	137.5
a fall propagation delay	204.6
b rise propagation delay	132.7
b fall propagation delay	203.0
c rise propagation delay	127.7
c fall propagation delay	202.6
d rise propagation delay	121.2
d fall propagation delay	198.0

System Verilog Simulation

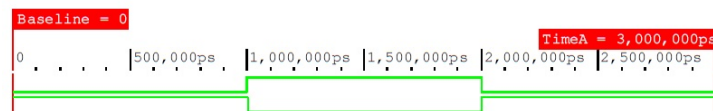


11 nor2


Designer: Henry Lovett

Cell Description: A two input NOR gate

Symbol

 


Dimensions

 

AC Characteristics

Signal	Delay (ps)
a rise prop delay	91.8
a fall prop delay	196.4
b rise prop delay	87.6
b fall prop delay	192.9

System Verilog Simulation

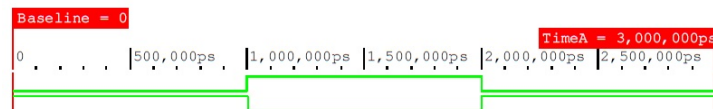


12 nor3


Designer: Henry Lovett

Cell Description: A three input NOR gate

Symbol

 


Dimensions

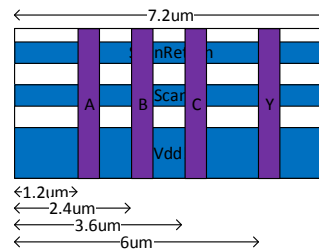

AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

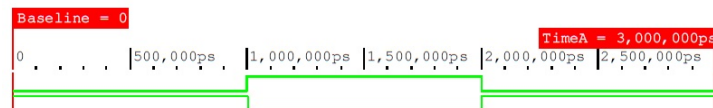


13 or2


Designer: Henry Lovett

Cell Description: A two input OR gate

Symbol

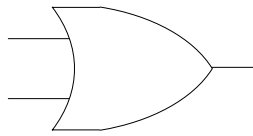


Dimensions

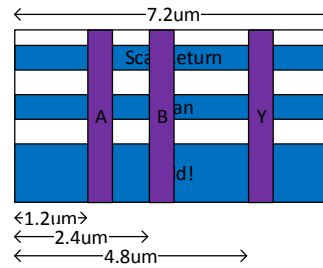

AC Characteristics

Signal	Delay (ps)
a fall delay	174.0
a rise delay	140.9
b fall delay	176.3
b rise delay	150.5


System Verilog Simulation

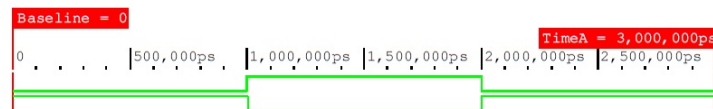


14 rightend

Designer: Henry Lovett
Cell Description: An end of row buffer cell.

Symbol

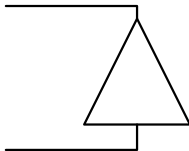


Dimensions

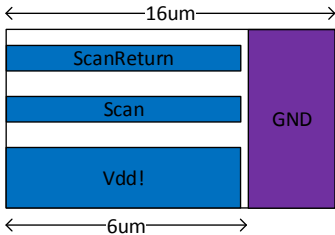

AC Characteristics

Signal	Delay (ps)
scan fall delay	56.4
scan rise delay	78.2

System Verilog Simulation

 


15 scandtype


Designer: Constantijn Schepens

Cell Description: A Raw DType cell

Symbol

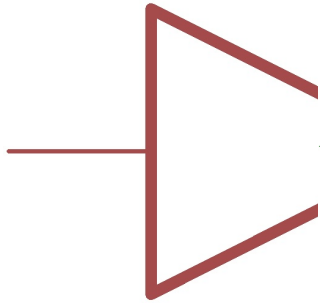

Circuit Diagram

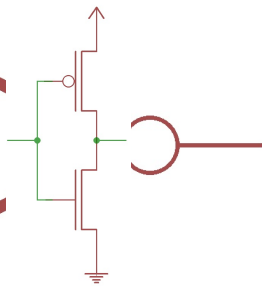


Dimensions



AC Characteristics

Signal	Delay (ps)
clock to q rise	336.9
clock to q fall	509.6
clock to nq rise	302.0
clock to nq fall	590.0
nreset to q fall	385.4
nreset to nq rise	177.7

System Verilog Simulation

 


16 scanreg


Designer: Constantijn Schepens

Cell Description: A Raw DType cell

Symbol

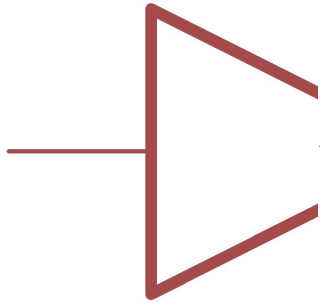

Circuit Diagram

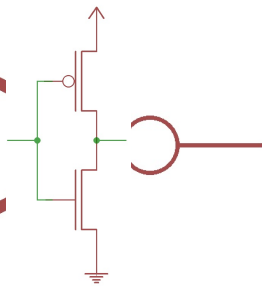


Dimensions



AC Characteristics

Signal	Delay (ps)
clock to q rise	357.2
clock to q fall	542.1
clock to nq rise	301.5
clock to nq fall	617.0
nreset to q fall	412.5
nreset to nq rise	178.3

System Verilog Simulation

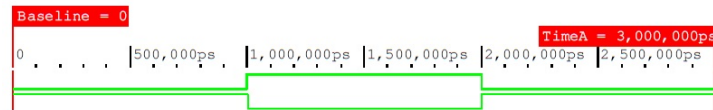


17 Rowcrosser

Designer: Martin Wearn

Cell Description: A row crossing cell.

Dimensions

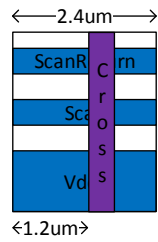


18 Tie High

Designer: Martin Wearn

Cell Description: A tie to Vdd cell.

Dimensions

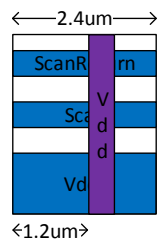


19 Tie Low

Designer: Martin Wearn

Cell Description: A tie low cell.

Dimensions

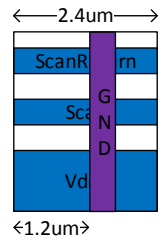


20 trisbuf


Designer: Ashley Robinson

Cell Description: A tristate buffer

Symbol

 

Circuit Diagram

 


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

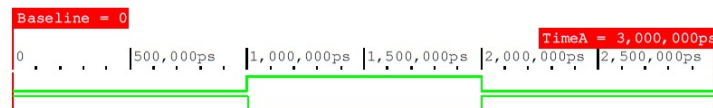

21 xor2


Designer: Ashley Robinson

Cell Description: A two input xor gate

Symbol

Circuit Diagram


Dimensions

 

AC Characteristics

Signal	Delay (ps)
prop delay a 1	305.0
prop delay a 2	241.7
prop delay b 1	184.3
prop delay b 2	201.7
average prop a	273.4
average prop b	193.0

System Verilog Simulation

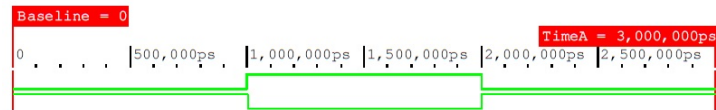

A Appendix A

A.1 Team Management

A.2 Division of Labour


B Design Detail

B.1 fulladder


Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bitslice carry out, to produce a sum and carry

Stick Diagram

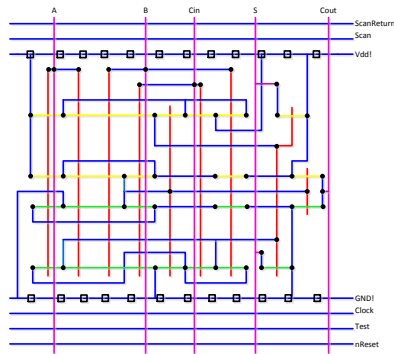

Transistor Level Circuit Diagram

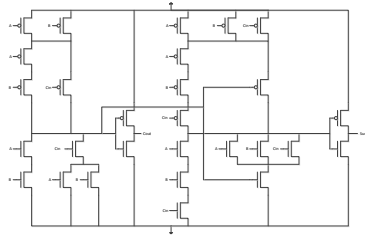


B.2 halfadder


Designer: Martin Wearn

Cell Description: Adds two bits to produce a sum and carry

Stick Diagram

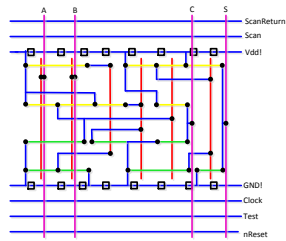

Transistor Level Circuit Diagram

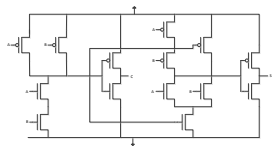


B.3 leftbuf


Designer: Henry Lovett

Cell Description: A start of row buffer cell.

Stick Diagram

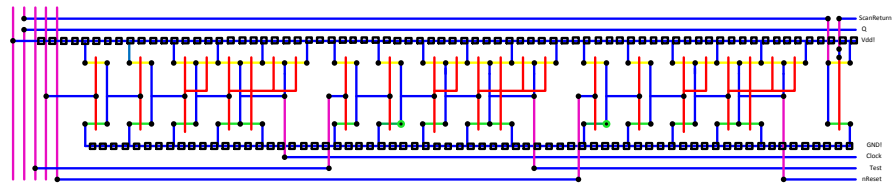

Transistor Level Circuit Diagram

 


B.4 rdtype


Designer: Ashley Robinson

Cell Description: Raw Dtype

Stick Diagram

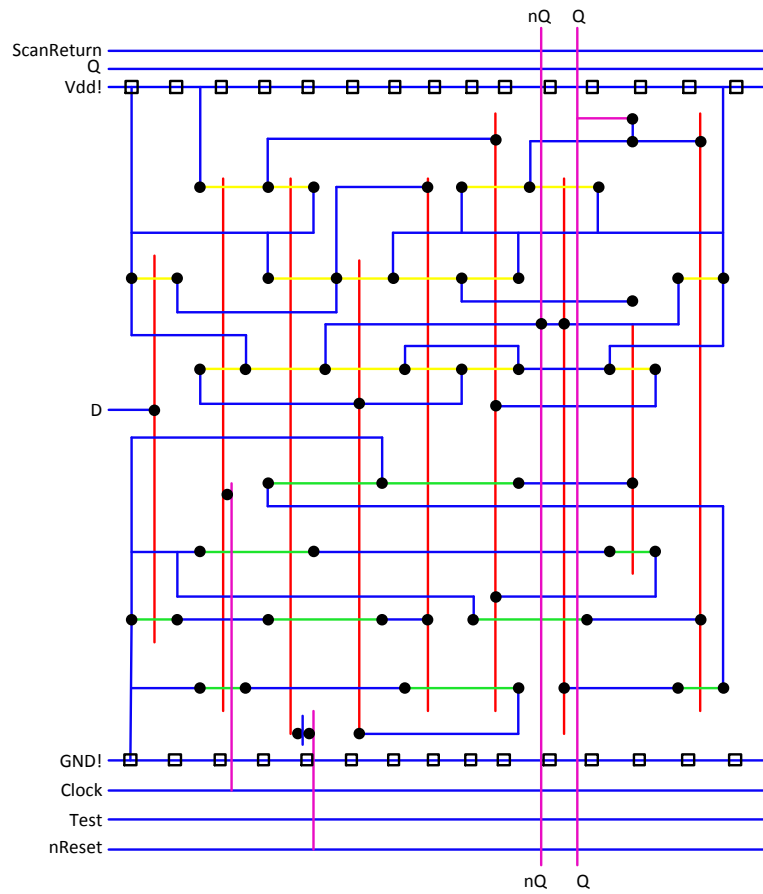

Transistor Level Circuit Diagram

 


B.5 smux2


Designer: Schep

Cell Description: A start of row buffer cell.

Stick Diagram

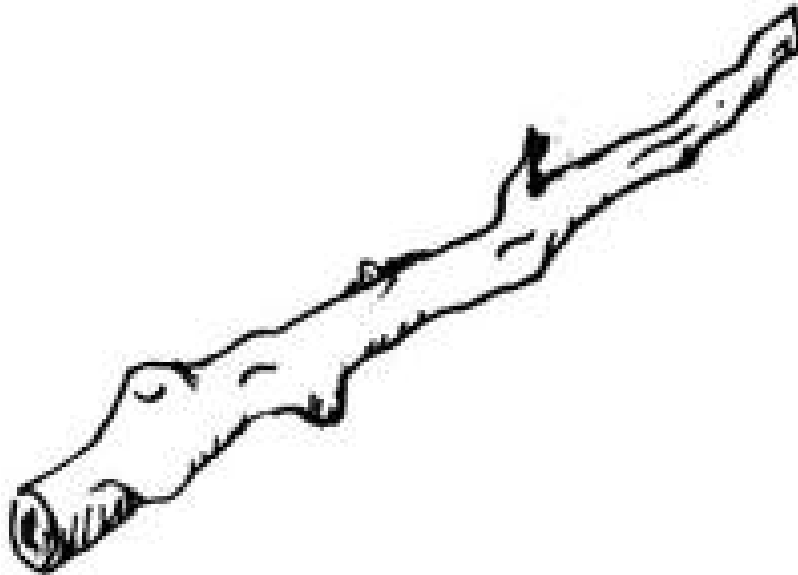

Transistor Level Circuit Diagram

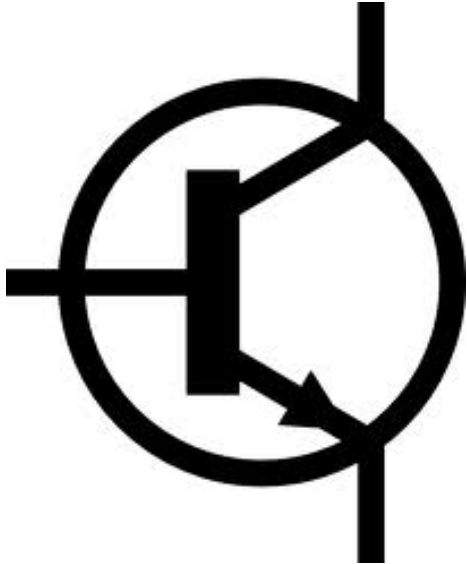


B.6 smux3


Designer: Schep

Cell Description: A scan multiplexor.

Stick Diagram

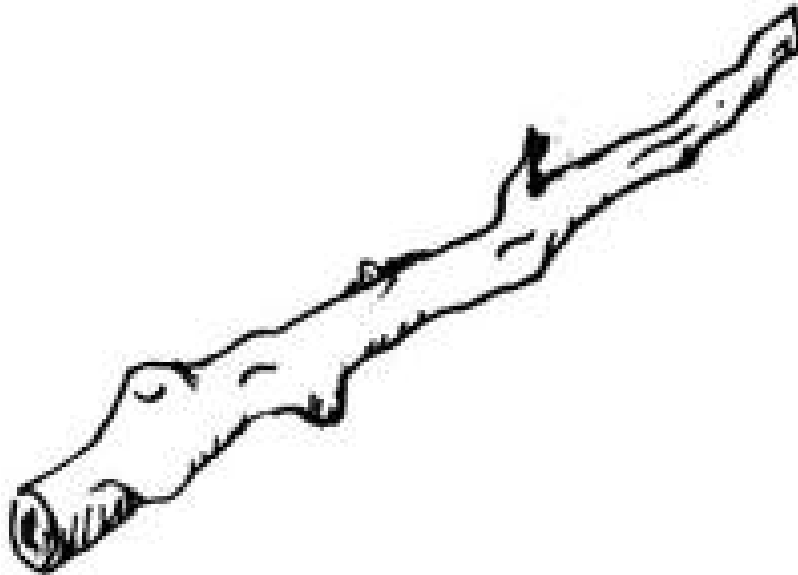

Transistor Level Circuit Diagram

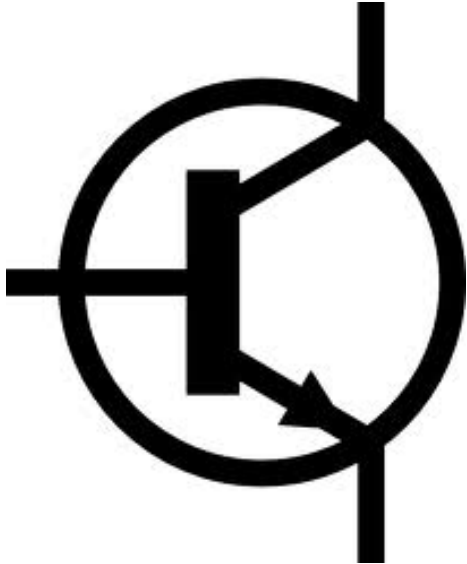


B.7 xor2

Designer: Ashley Robinson

Cell Description: A 2 input XOR gate.

Stick Diagram

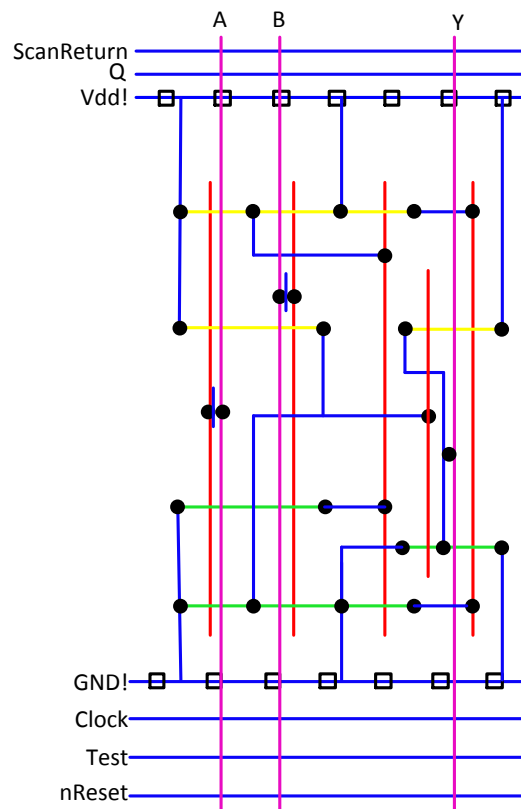

Transistor Level Circuit Diagram

