

Cell Library Databook

by Team S5

H. Lovett (hl13g10)

A. J. Robinson (ajr2g10)

C. Schepens (cs7g10)

M. Wearn (mw20g10)


December 3, 2013

And2


Designer: Constantijn Schepens

Cell Description: A two input AND gate

Symbol

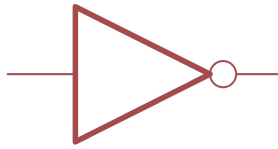

Circuit Diagram

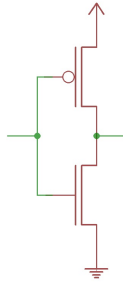


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

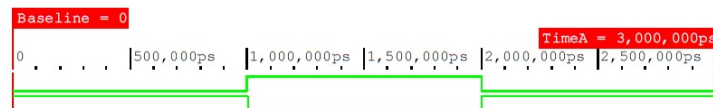


buffer


Designer: Ashley Robinson

Cell Description: A non-inverting buffer

Symbol

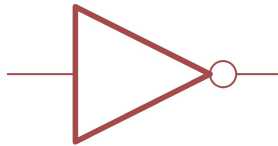

Circuit Diagram

 


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

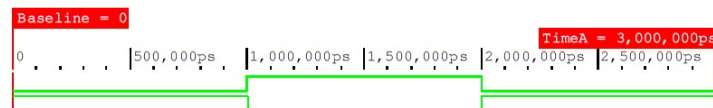


fulladder


Designer: Martin Wearn

Cell Description: A Full Adder

Symbol

 

Circuit Diagram

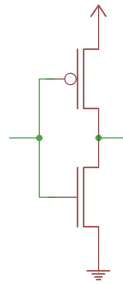


Dimensions



AC Characteristics




Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

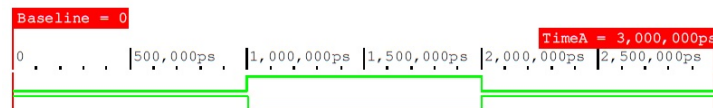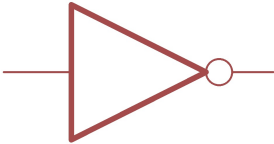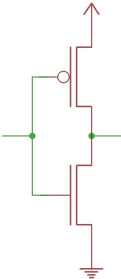

halfadder


Designer: Martin Wearn
Cell Description: A Half Adder

Symbol	Circuit Diagram	Dimensions
		

AC Characteristics

Signal	Delay (s)
TO BE	DONE


System Verilog Simulation

 


Inverter

Designer: Henry Lovett
Cell Description: A basic inverter gate


Symbol

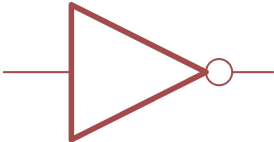

Circuit Diagram

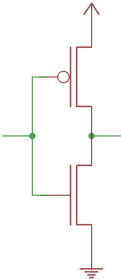


Dimensions



AC Characteristics

Signal	Delay (s)
a rise delay	1.306e-10
a fall delay	9.373e-11

System Verilog Simulation

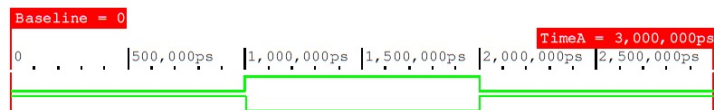


leftbuf


Designer: Henry Lovett

Cell Description: A start of row buffer cell.

Symbol

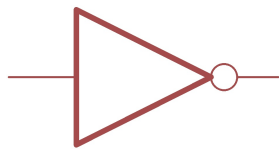

Circuit Diagram

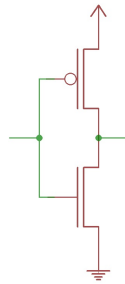


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

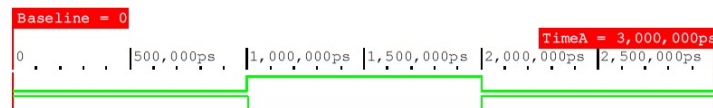


mux2


Designer: Constantijn Schepens

Cell Description: A two input Multiplexor

Symbol

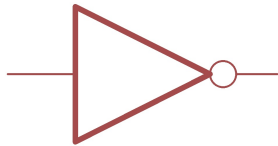

Circuit Diagram

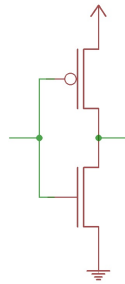


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

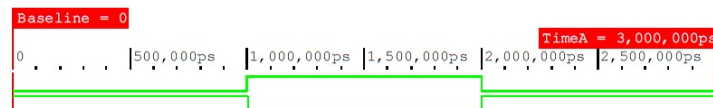


nand2


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

 

Circuit Diagram

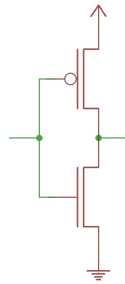


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

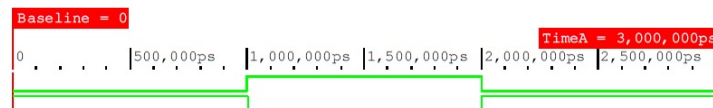


nand3


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

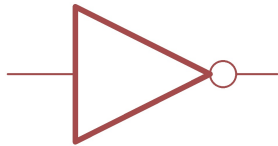

Circuit Diagram

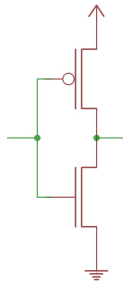


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

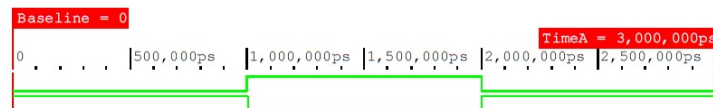


nand4


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

 

Circuit Diagram

 


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

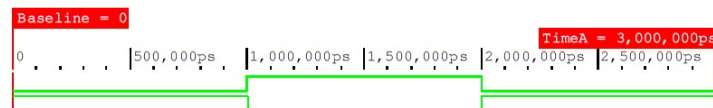


nor2


Designer: Henry Lovett

Cell Description: A two input NOR gate

Symbol

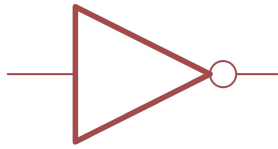

Circuit Diagram

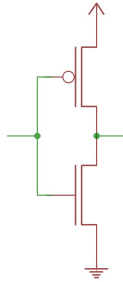


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

 


nor3


Designer: Henry Lovett

Cell Description: A three input NOR gate

Symbol

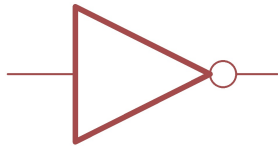

Circuit Diagram

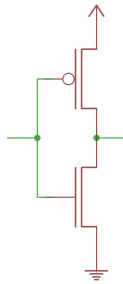


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

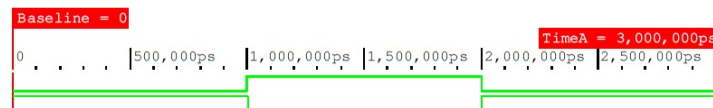


or2


Designer: Henry Lovett

Cell Description: A two input OR gate

Symbol

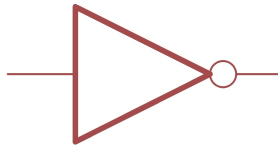

Circuit Diagram

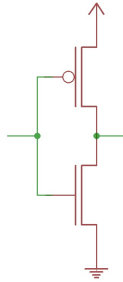


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

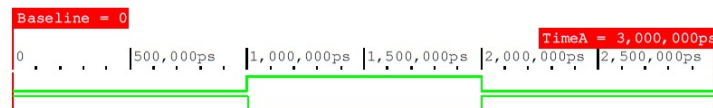


rightend


Designer: Henry Lovett

Cell Description: An end of row buffer cell.

Symbol

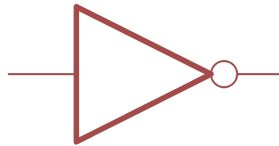

Circuit Diagram

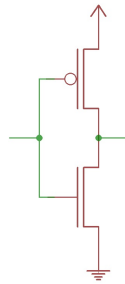


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

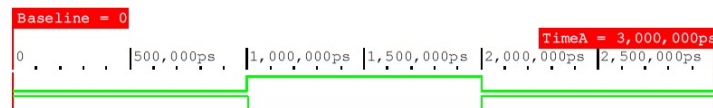


rowcrosser


Designer: Martin Wearn
Cell Description: A rowcrossing cell


Symbol

Circuit Diagram

Dimensions

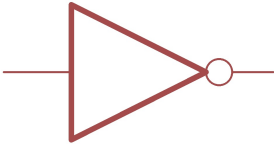

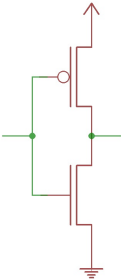




AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

 


scandtype


Designer: Constantijn Schepens

Cell Description: A Raw DType cell

Symbol

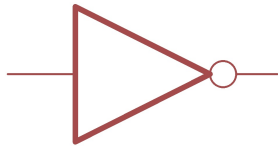

Circuit Diagram

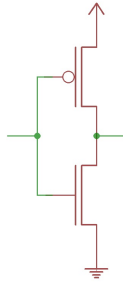


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

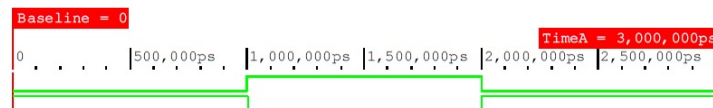


scanreg


Designer: Constantijn Schepens

Cell Description: A Raw DType cell


Symbol

 

Circuit Diagram

 


Dimensions

 

AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

 


tiehigh


Designer: Martin Wearn

Cell Description: A tie to Vdd cell

Symbol

 

Circuit Diagram

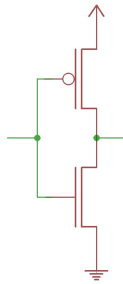


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

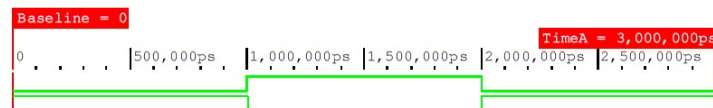


tielow


Designer: Martin Wearn

Cell Description: A tie to GND cell

Symbol

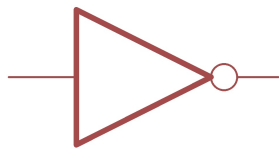

Circuit Diagram

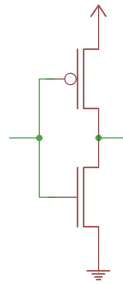


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

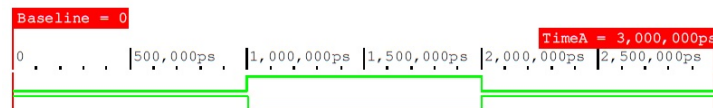


trisbuf


Designer: Ashley Robinson

Cell Description: A tristate buffer

Symbol

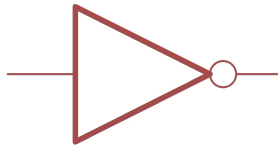

Circuit Diagram

 


Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

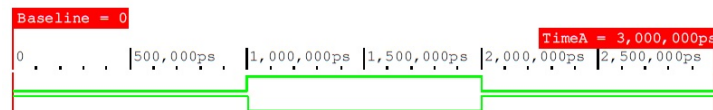


xor2


Designer: Ashley Robinson

Cell Description: A two input xor gate

Symbol

 

Circuit Diagram

 

Dimensions



AC Characteristics

Signal	Delay (s)
TO BE	DONE

System Verilog Simulation

