

Cell Library Databook

by Team S5

H. Lovett (hl13g10)

A. J. Robinson (ajr2g10)

C. Schepens (cs7g10)

M. Wearn (mw20g10)

December 10, 2013

Contents

1 AND2	6
2 BUFFER	7
3 FULLADDER	8
4 HALFADDER	10
5 INV	12
6 LEFTBUF	13
7 MUX2	15
8 NAND2	17
9 NAND3	18
10 NAND4	19
11 NOR2	20
12 NOR3	21
13 OR2	22
14 RIGHTEND	24
15 SCANDTYPE	26
16 SCANREG	28
17 TIE HIGH	29
18 TIE LOW	29
19 ROWCROSSER	29
20 TRISBUF	31
21 XOR2	33
A Appendix A	35
A.1 Team Management	35
A.1.1 Justification of the Division of Labour	35
A.1.2 Version Control	35
A.1.3 Process automation	35

A.2	Division of Labour	36
B	Design Detail	37
B.1	FULLADDER	38
B.2	HALFADDER	40
B.3	LEFTBUF	42
B.4	RDTYPE	44
B.5	SMUX2	46
B.6	SMUX3	48
B.7	XOR2	51

Introduction

The set of cells contained within this library are based upon $0.35\mu m$ unified CMOS technology. They follow a two-layer metal design on top of a p-type substrate with N-Well and P-Well regions for pull-up and pull-down networks respectively. All cells are a common $17.2\mu m$ high, with varied widths all integer multiples of $1.2\mu m$. All transistors are fixed at $W_P = 2.4\mu m$, $L_P = 0.35\mu m$, $W_N = 1.5\mu m$, $L_N = 0.35\mu m$.

Global signals and power rails are arranged horizontally in *metal1*. Figure 1 shows this arrangement with the dimensions of the global signals. While cell I/O signals are arranged vertically in *metal2* and aligned to a $1.2\mu m$ grid. Power rails are $1.25\mu m$ wide, while other horizontal signals are $0.5\mu m$ wide. The distance between horizontal signals is $0.8\mu m$ from centre to centre. Both rails are formed using a continuous ohmic region and line of taps.

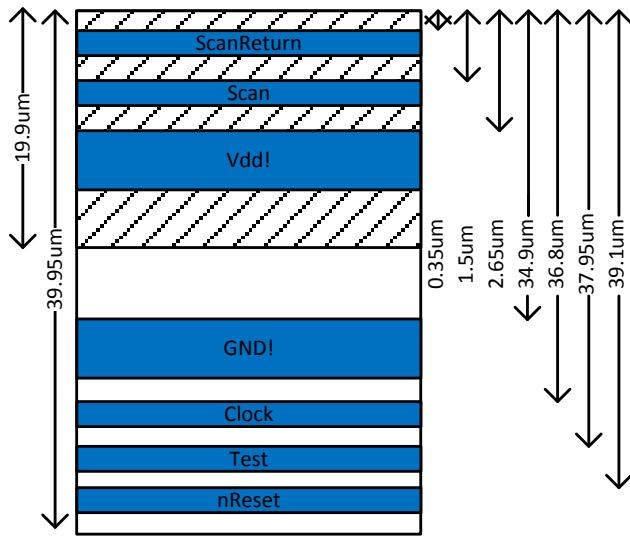


Figure 1: Global signals common to all cells

Vertical signals lines are $0.6\mu m$ wide with position of each signal measured from the left edge of the cell to the right edge of the metal strip and detailed on each cell page.

AC characteristics of cells are measured as the propagation delay from each input to each output under normal operation conditions. This is set as having each input driven through one inverter and each output loaded by two inverters from this library. Each cell lists both the delay to correct output as a result of an input going high, as well as an input going low.

Major cells in the library have additional sections detailing the stick diagram and transistor layout of each cell as designed by the designated team member. Even though only 4 members were in the group, both the half adder and XOR2 have been included in the library and detailed.



1 AND2

Designer: Constantijn Schepens


Cell Description: A two input AND gate

Dimensions

Symbol

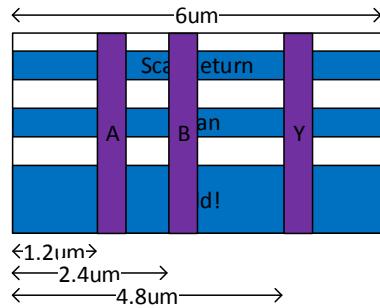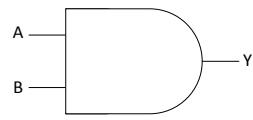


Gate Level Diagram

 

AC Characteristics

Signal	Average Delay (ps)
a to y	121.7
b to y	124.0


System Verilog Simulation

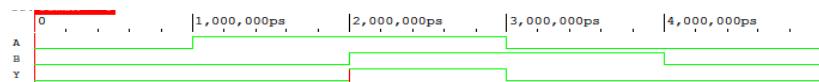


2 BUFFER

Designer: Ashley Robinson

Cell Description: A non-inverting buffer

 


Gate Level Diagram

 

AC Characteristics

Signal	Average Delay (ps)
a to y	134.2

System Verilog Simulation

 


3 FULLADDER


Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bits crie carry out, to produce a sum and carry


Symbol

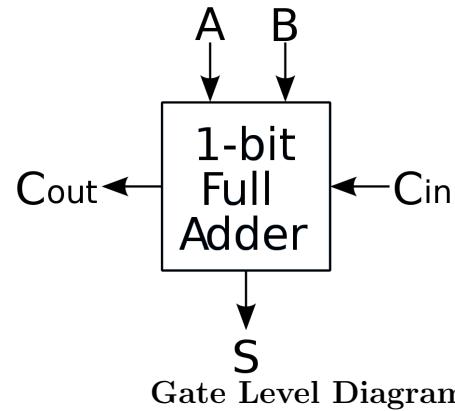

Dimensions

 

Gate Level Diagram

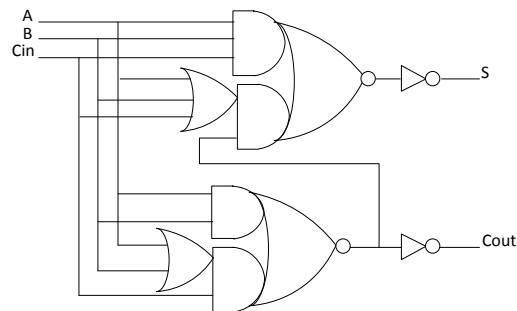

AC Characteristics

System Verilog Simulation

Signal	Average Delay (ps)
a to s	294.9
a to cout	285.0
b to s	262.3
b to cout	294.0
cin to s	252.7
cin to cout	274.6




4 HALFADDER



Designer: Martin Wearn

Cell Description: Adds two bits to produce a sum and carry

Symbol

 


Dimensions

  

AC Characteristics

Signal	Average Delay (ps)
a to s	251.7
a to c	167.0
b to s	240.9
b to c	166.1

System Verilog Simulation

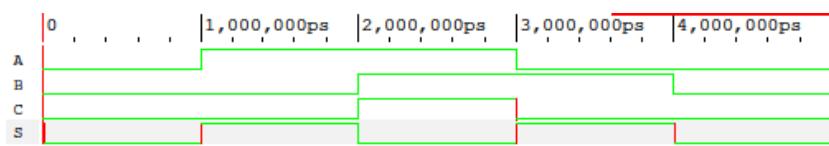


5 INV


Designer: Henry Lovett

Cell Description: A basic inverter gate

Symbol

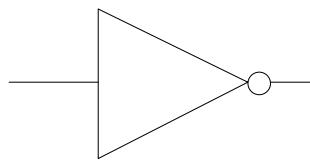


Dimensions

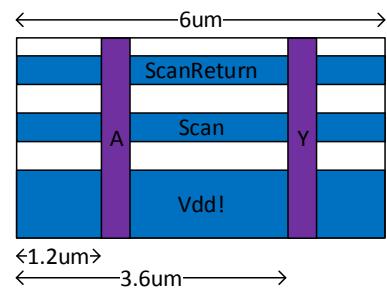

AC Characteristics

Signal	Average Delay (ps)
a to y	94.5

System Verilog Simulation

 


6 LEFTBUF


Designer: Henry Lovett

Cell Description: A start of row buffer cell.


Symbol

 

Dimensions

 


Gate Level Diagram

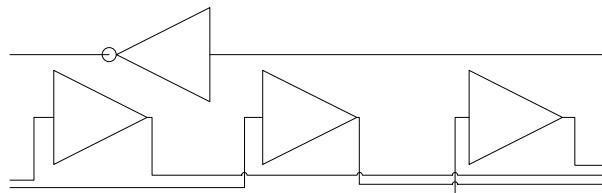

AC Characteristics

Signal	Average Delay (ps)
clock to clockout	279.4
test to testout	277.6
nreset to nresetout	281.9
nsdo to sdo	141.2

System Verilog Simulation

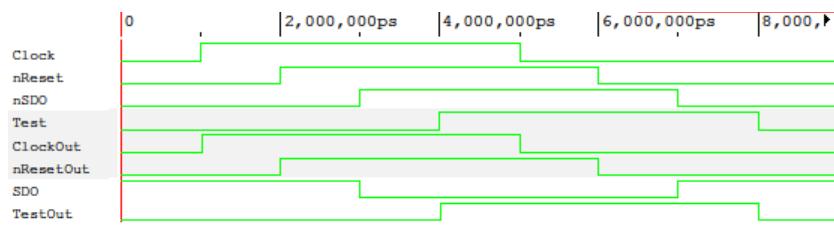


7 MUX2


Designer: Constantijn Schepens

Cell Description: A two input Multiplexor


Symbol

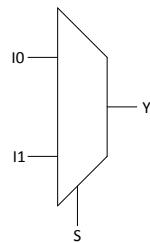

Dimensions

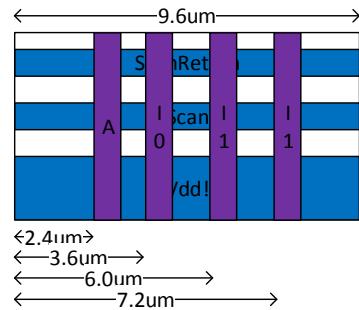


Gate Level Diagram

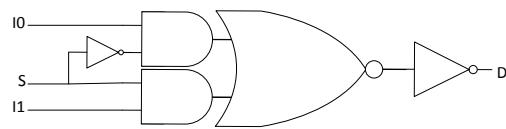

AC Characteristics

Signal	Average Delay (ps)
i0 to d	182.5
i1 to d	213.0
s pass i0 propagation	214.0
s pass i1 propagation	224.7

System Verilog Simulation

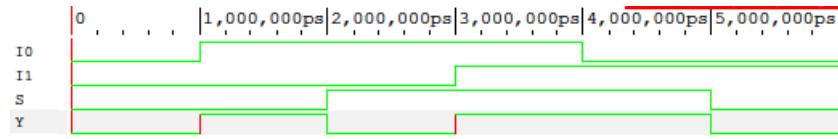


8 NAND2


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

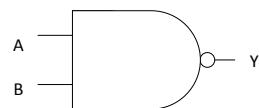


Dimensions

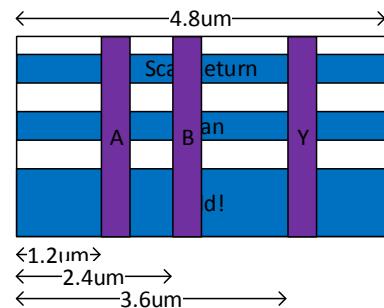

AC Characteristics

Signal	Average Delay (ps)
a to y	117.0
b to y	117.6

System Verilog Simulation

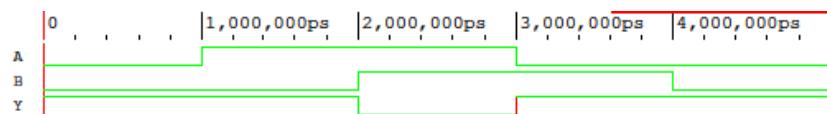


9 NAND3

Designer: Constantijn Schepens

Cell Description: A three input NAND gate

Dimensions

Symbol

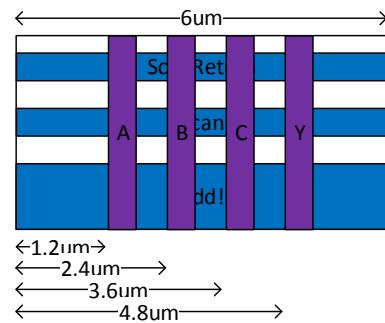

AC Characteristics

Signal	Average Delay (ps)
a to y	142.8
b to y	142.3
c to y	137.5

System Verilog Simulation





10 NAND4

Designer: Constantijn Schepens

Cell Description: A four input NAND gate

Dimensions


Symbol

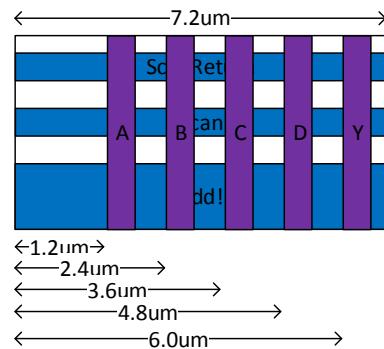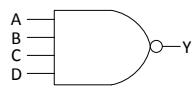

AC Characteristics

Signal	Average Delay (ps)
a to y	171.0
b to y	167.9
c to y	165.1
d to y	159.6

System Verilog Simulation

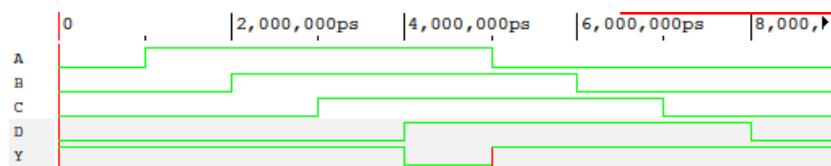


11 NOR2


Designer: Henry Lovett

Cell Description: A two input NOR gate

Symbol

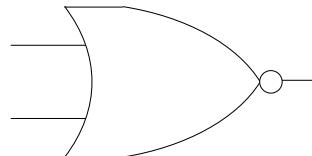


Dimensions

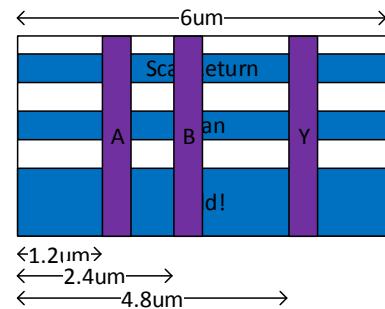

AC Characteristics

Signal	Average Delay (ps)
a to y	144.1
b to y	140.2

System Verilog Simulation

 


12 NOR3


Designer: Henry Lovett

Cell Description: A three input NOR gate

Symbol

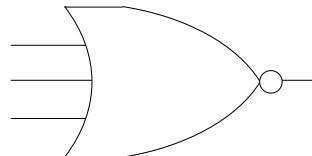

Dimensions

 

AC Characteristics

Signal	Average Delay (ps)
a to y	203.1
b to y	185.4
c to y	198.1

System Verilog Simulation




13 OR2


Designer: Henry Lovett

Cell Description: A two input OR gate


Symbol

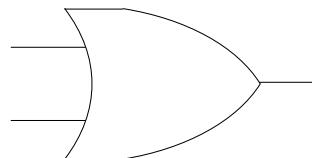

Dimensions

 


Gate Level Diagram

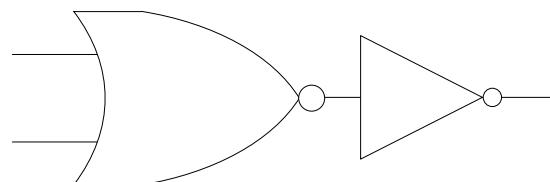

AC Characteristics

Signal	Average Delay (ps)
a to y	157.4
b to y	163.4

System Verilog Simulation

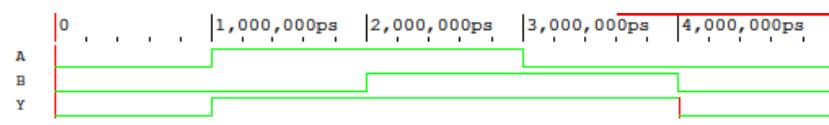


14 RIGHTEND


Designer: Henry Lovett

Cell Description: An end of row buffer cell.


Symbol

 

Dimensions

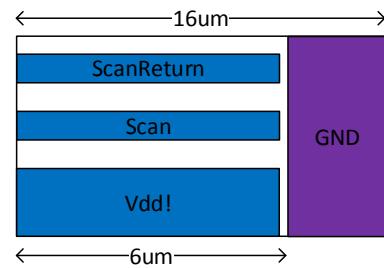


Gate Level Diagram

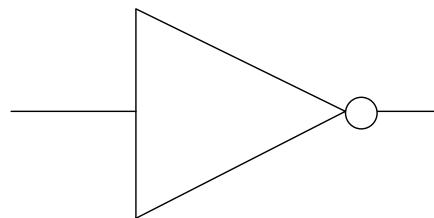

AC Characteristics

Signal	Average Delay (ps)
nsdo to sdo	67.3

System Verilog Simulation

 


15 SCANDTYPE


Designer: Constantijn Schepens

Cell Description: A scannable D-Type cell


Symbol

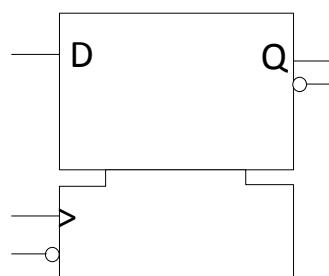

Dimensions

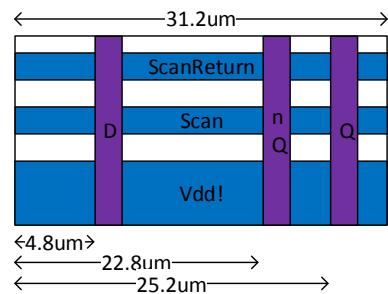


Gate Level Diagram

 

AC Characteristics

Signal	Average Delay (ps)
clock to q	423.3
clock to nq	446.0
nreset to clear	281.5

System Verilog Simulation

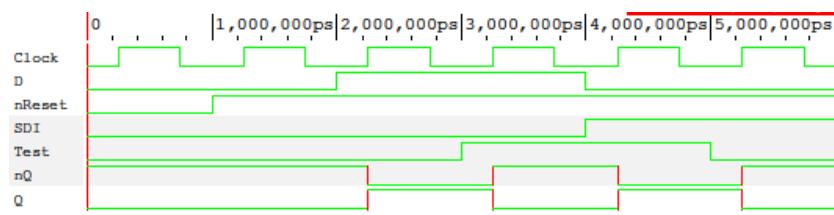


16 SCANREG


Designer: Constantijn Schepens

Cell Description: A scannable register cell


Symbol

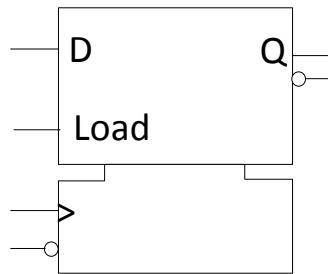

Dimensions

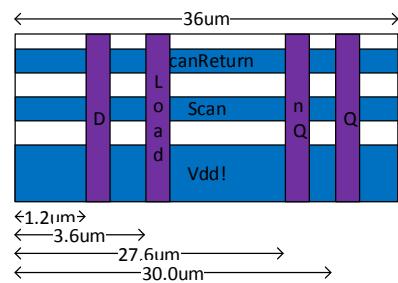

Gate Level Diagram

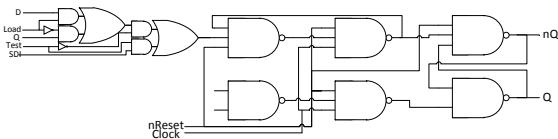

AC Characteristics

Signal	Average Delay (ps)
clock to q	449.6
clock to nq	459.3
nreset to clear	295.4


System Verilog Simulation



17 TIE HIGH

Designer: Martin Wearn
Cell Description: A tie to Vdd cell.


Dimensions

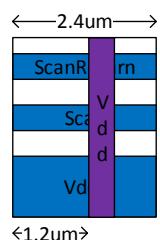

18 TIE LOW

Designer: Martin Wearn
Cell Description: A tie to GND cell.


Dimensions

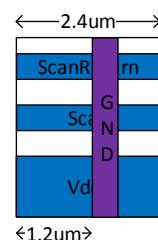

19 ROWCROSSEr

Designer: Martin Wearn
Cell Description: A row crossing cell.


Dimensions

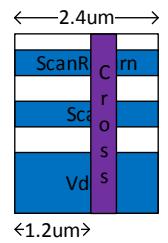


20 TRISBUF

Designer: Ashley Robinson
Cell Description: A tristate buffer

Symbol **Dimensions**

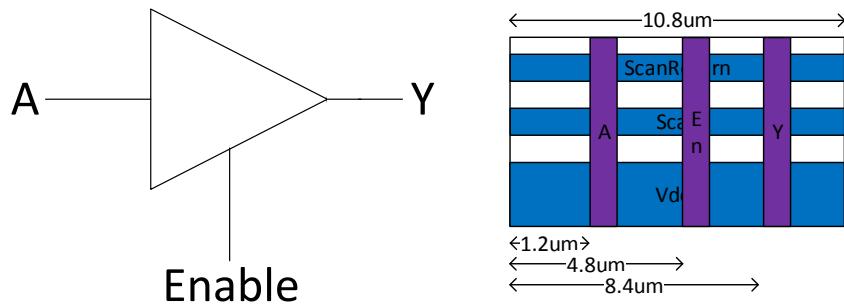

Gate Level Diagram

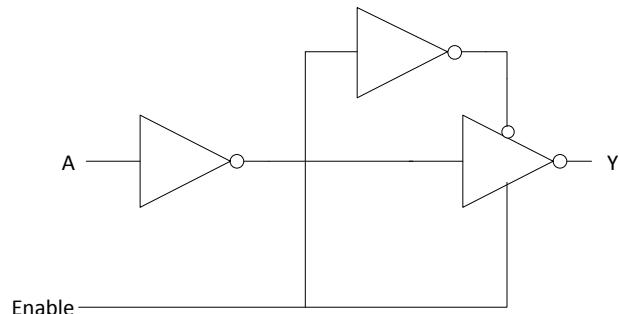

AC Characteristics

Signal	Average Delay (ps)
a to y	211.8

System Verilog Simulation




21 XOR2


Designer: Ashley Robinson

Cell Description: A two input xor gate


Symbol

 

Dimensions

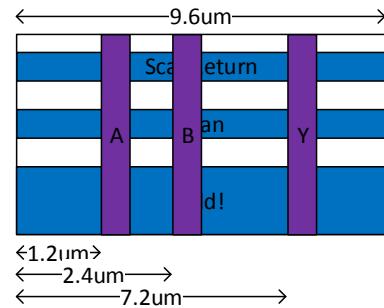


Gate Level Diagram

 

AC Characteristics

Signal	Average Delay (ps)
a to y	273.4
b to y	193.0

System Verilog Simulation

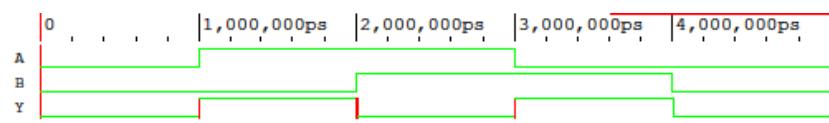

A Appendix A

A.1 Team Management

A.1.1 Justification of the Division of Labour

The four major cells were divided between the team as recommended in the specification. It was decided to also attempt the optional cells for teams of four. An extra person in a team of five would be in charge of designing the halfadder and xor2. The halfadder was assigned to the team member designing the fulladder as their expertise was greater for designing adder cells. The xor2 cell was assigned to the team member designing the rdtype as this cell was assumed less time consuming than the two other sets of major cells. The remaining cells were grouped and divided among the teams as shown in Table 1.

Cell Groupings	Reasoning
and2, and2, nand3, nand4	Nands and Ands are similar in design.
buffer, trisbuf	Buffers are similar in design.
inverter, nor2, nor3, or2	Nors and Ors similar in design. Inverter is a simple cell assigned to distribute load.
rowcrosswer, tiehigh, tielow	Low complexity cells assigned to team member tasked with designing both adders.

Table 1: Cell design groupings and reasoning

A.1.2 Version Control

The Git revision control system was used throughout the project to facilitate collaborative working. GitHub is a web-based hosting service for git. This was used to share files, allocate work and track bugs.

A.1.3 Process automation

The team produced a number of scripts to improve productivity by automating processes such extraction from magic, design simulation and consistency checking. Using Latex allowed the databook compilation to also be automated as separate files for each cell were stored in the hierarchy of folders. This way each designer could add their own files to the data book independently.

A.2 Division of Labour

	Task	Percentage Effort on Each Task (%)			
	ECS ID	mw20g10	cs7g10	ajr2g10	hl13g10
1	RDTYPE	0	0	100	0
2	SMUX2	0	100	0	0
3	SMUX3	0	100	0	0
4	MUX2	0	100	0	0
5	FULLADDER	100	0	0	0
6	HALFADDER	100	0	0	0
7	XOR2	0	0	100	0
8	INV	0	0	0	100
9	NAND2	0	100	0	0
10	NAND3	0	100	0	0
11	NAND4	0	100	0	0
12	NOR2	0	0	0	100
13	NOR3	0	0	0	100
14	AND2	0	100	0	0
15	OR2	0	0	0	100
16	TRISBUF	0	0	100	0
17	BUFFER	0	0	100	0
18	LEFTBUF	0	0	0	100
19	RIGHTEND	0	0	0	100
20	TIEHIGH	100	0	0	0
21	TIELOW	100	0	0	0
22	ROWCROSSER	100	0	0	0
23	SCANDTYPE	0	0	0	0
24	SCANREG	0	0	0	0
25	Verilog Simulation	0	0	0	0
26	HSpice Characterization	0	0	0	0
27	Final Report (words)	0	0	0	0
28	Final Report (figures)	0	0	0	0
	OVERALL EFFORT	0	0	0	0
	Signature:				


B Design Detail

B.1 FULLADDER

Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bitslice carry out, to produce a sum and carry


Stick Diagram

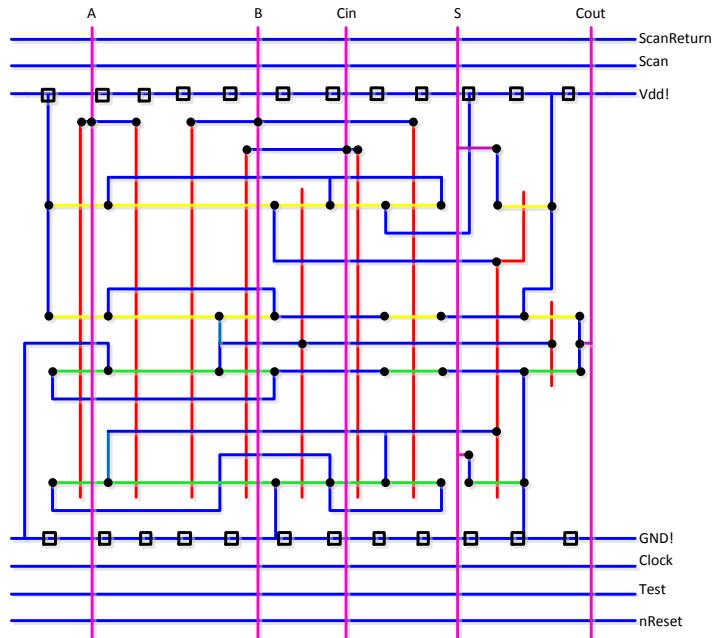


AC Characteristics

Signal	Average Delay (ps)
a to s	294.9
a to cout	285.0
b to s	262.3
b to cout	294.0
cin to s	252.7
cin to cout	274.6

Transistor Level Circuit Diagram

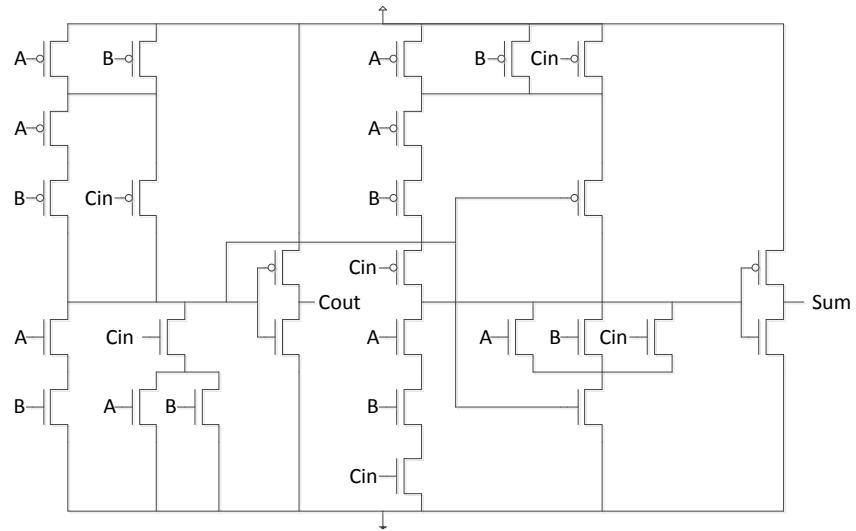

HSpice Simulation

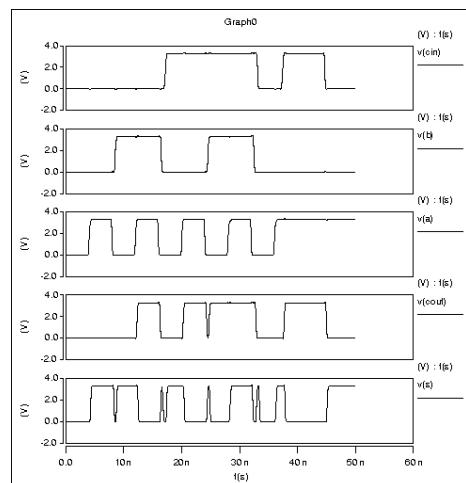


B.2 HALFADDER

Designer: Martin Wearn

Cell Description: Adds two bits to produce a sum and carry


Stick Diagram

 


AC Characteristics

Signal	Average Delay (ps)
a to s	251.7
a to c	167.0
b to s	240.9
b to c	166.1

Transistor Level Circuit Diagram

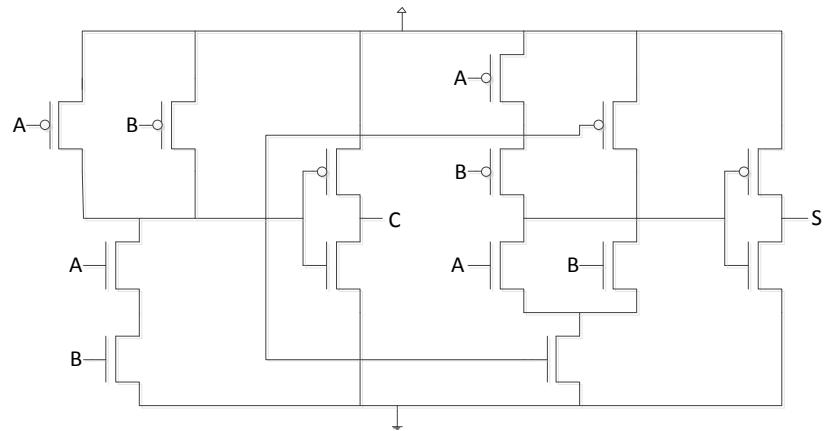

HSpice Simulation

 

B.3 LEFTBUF

Designer: Henry Lovett


Cell Description: A start of row buffer cell.

This cell is to be placed at the beginning of each row of cells. The purpose of this cell is to buffer the *Clock*, *nReset* and *Test* signals to attempt to eliminate skew of the signals. They also cater for the scan path in the circuit by routing and buffering the signal.

This cell contains 3 large buffers, each made up of 4 stages. The gain of the stages are gradually increased, relative to the first. The transistors were folded to reduce the vertical height of the cell. The total, and folded sizes of the transistors are seen in the table below.

Stage	1	2	3	4
Gain	1	2.7	7.3	20
W_n unfolded (μm)	1.0	2.7	7.3	20
W_p unfolded (μm)	2.9	7.85	21.2	58
W_n folded (μm)	1×1.0	1×2.7	1×7.3	2×10.0
W_p folded (μm)	1×2.9	1×7.85	2×10.6	4×14.5


Stick Diagram

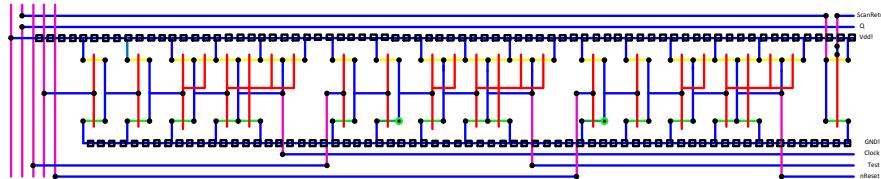


AC Characteristics

Signal	Average Delay (ps)
clock to clockout	279.4
test to testout	277.6
nreset to nresetout	281.9
nsdo to sdo	141.2

Transistor Level Circuit Diagram

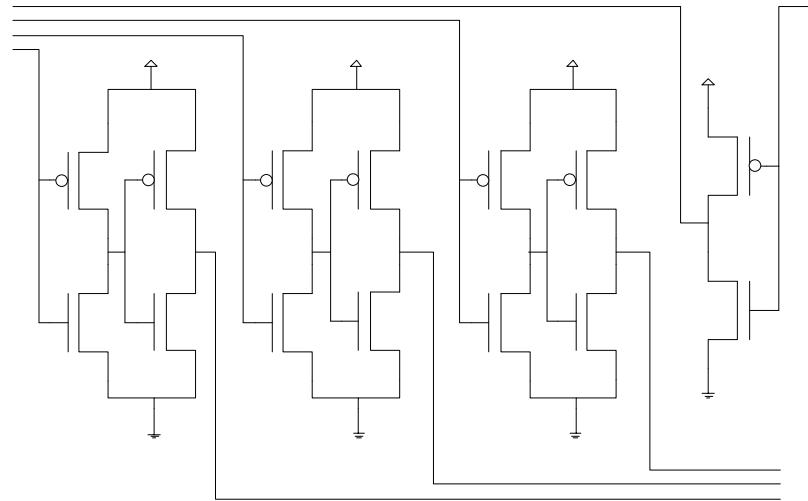

HSpice Simulation

 


B.4 RDTYPE

Designer: Ashley Robinson
Cell Description: Raw Dtype

This gate matrix design was optimised by arranging polysilicon columns to allow as many transistors to fit on a row as possible. Three rows of PMOS transistors and four rows of NMOS transistors make up cell. Routing power rails up both sides of the matrix allowed the design to be further compressed. The D input on the middle left was intentionally not surrounded leaving only metal1 to reroute when it came to dimension matching.


Stick Diagram

 


AC Characteristics

Signal	Average Delay (ps)
TO BE	DONE

Transistor Level Circuit Diagram

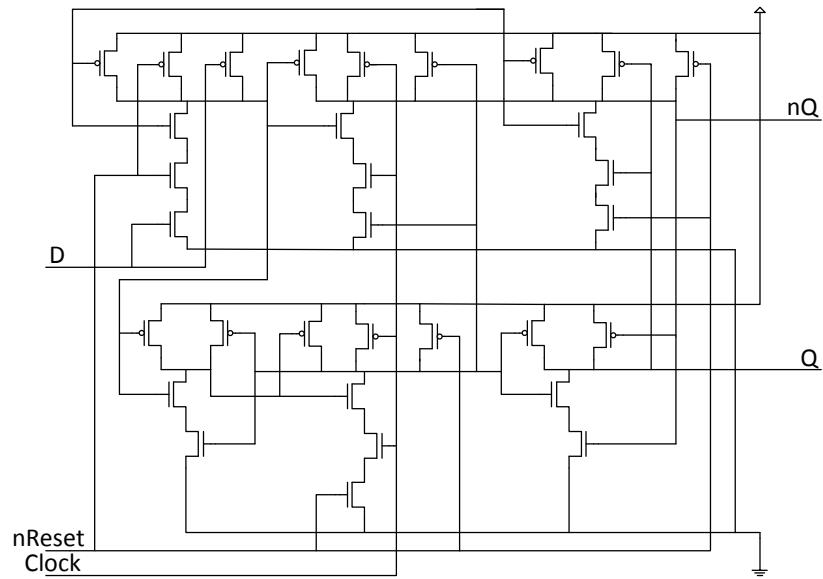

HSpice Simulation

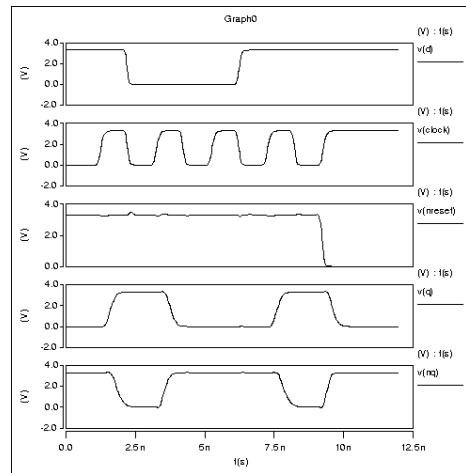


B.5 SMUX2

Designer: Constantijn Schepens

Cell Description: A 2 input scannable multiplexer, intended to be connected to a raw D-type to create a scannable D-type.

A single Euler path was used when laying out this cell, before taking into account inverters. The Euler path (T-nT-D-S) was designed such that the output was all the way on the right side such that it could connect directly to the D input of the raw D-type. Once this was done the required internal inverters were added in by creating a gate matrix design.


Stick Diagram

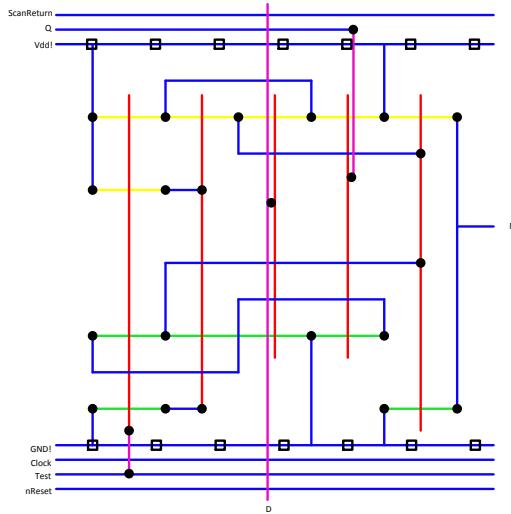


AC Characteristics

Signal	Average Delay (ps)
sdi propagation	212.5
d propagation	182.1
test pass sdi propagation	223.5
test pass d propagation	213.8

Transistor Level Circuit Diagram

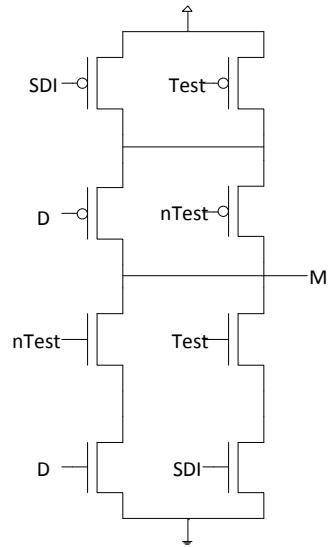

HSpice Simulation

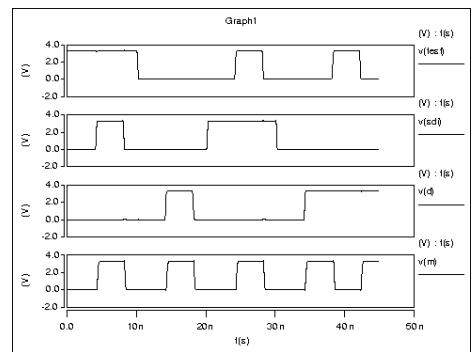


B.6 SMUX3

Designer: Constantijn Schepens

Cell Description: A 3 input scannable multiplexer, intended to be connected to a raw D-type to create a scannable register.

A similar approach was taken for the layout of this cell as for the smux2. Initially inverters were excluded and a single Euler path (D-Load-nTest-Test-SDI-nLoad-Q) was found that both kept M and Q as close to the right side as possible (to connect to the raw D-type) and kept the Test/Load nearest to their inverted partners for easy wiring. For the internal inverter placement multiple layouts were trialed to find the most efficient one, that also allowed all the internal wiring to be done with metal 1 exclusively(to reduce the number of vias).


Stick Diagram

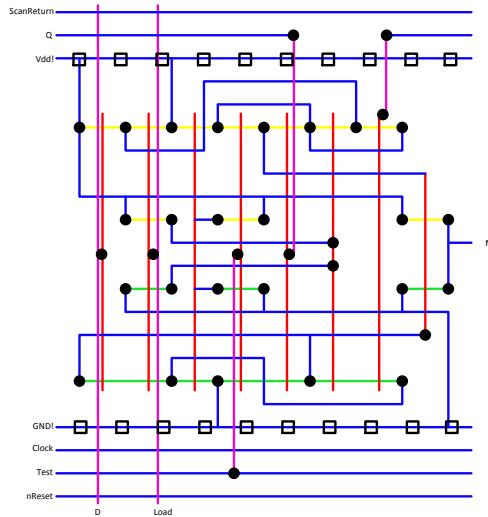


Signal	Average Delay (ps)
sdi propagation	227.0
d propagation	289.4
q propagation	259.1
test pass sdi propagation	242.9
test pass d propagation	287.0
test pass q propagation	278.9
load pass d propagation	296.1
load pass q propagation	303.6

AC Characteristics

Transistor Level Circuit Diagram

 

HSpice Simulation

 


B.7 XOR2

Designer: Ashley Robinson

Cell Description: A 2 input XOR gate.

Compound gate routed using an Euler path.


Stick Diagram

 

AC Characteristics

Signal	Average Delay (ps)
a to y	273.4
b to y	193.0

Transistor Level Circuit Diagram

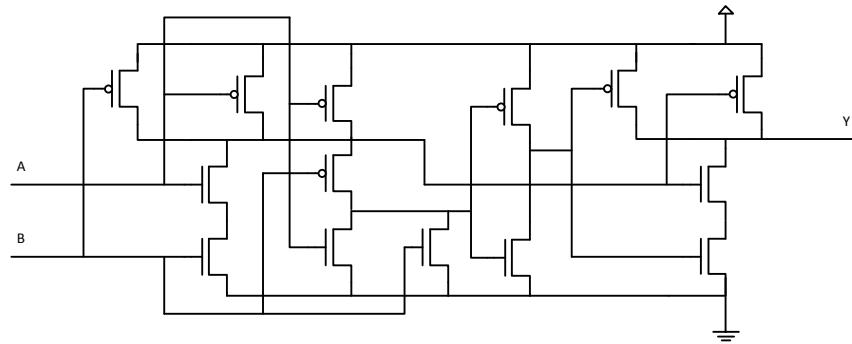

HSpice Simulation

