

Cell Library Databook

by Team S5

H. Lovett (hl13g10)

A. J. Robinson (ajr2g10)

C. Schepens (cs7g10)

M. Wearn (mw20g10)

December 9, 2013

Contents

1	And2	4
2	buffer	5
3	fulladder	6
4	halfadder	7
5	Inverter	8
6	leftbuf	9
7	mux2	10
8	nand2	11
9	nand3	12
10	nand4	13
11	nor2	14
12	nor3	15
13	or2	16
14	rightend	17
15	rowcrosser	18
16	scandtype	19
17	scanreg	20
18	tiehigh	21
19	tielow	22
20	trisbuf	23
21	xor2	24
A	Appendix A	25
A.1	Team Management	25
A.2	Division of Labour	26


B	Design Detail	27
B.1	fulladder	28
B.2	halfadder	30
B.3	leftbuf	31
B.4	rdtype	32
B.5	smux2	34
B.6	smux3	36
B.7	xor2	38

1 And2


Designer: Constantijn Schepens

Cell Description: A two input AND gate

Symbol

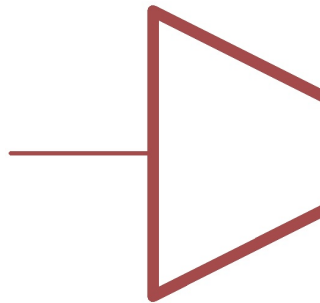

Circuit Diagram

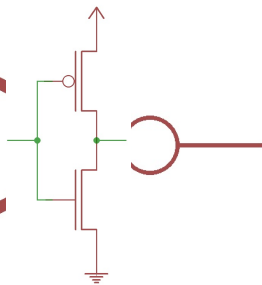


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

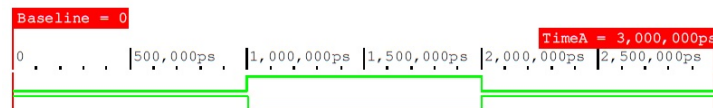


2 buffer


Designer: Ashley Robinson

Cell Description: A non-inverting buffer

Symbol

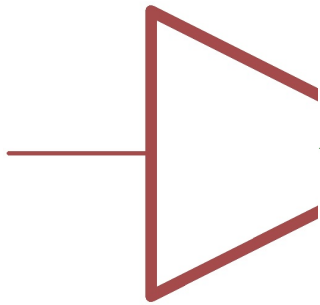

Circuit Diagram

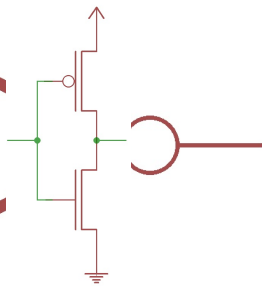


Dimensions



AC Characteristics

Signal	Delay (ps)
A to Y	134.2

System Verilog Simulation

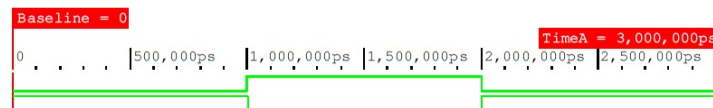


3 fulladder

Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bitscie carry out, to produce a sum and carry


Symbol

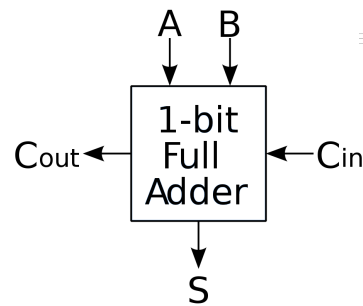

Circuit Diagram




Dimensions

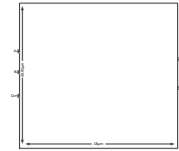

AC Characteristics

A to S/Cout prop delay (tPA) 331.7ps B to S/Cout prop delay (tPB) 358.3ps Cin to S/Cout prop delay (tP

System Verilog Simulation

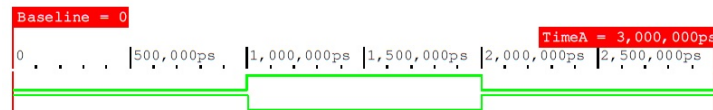


4 halfadder

Designer: Martin Wearn


Cell Description: Adds two bits to produce a sum and carry

Symbol

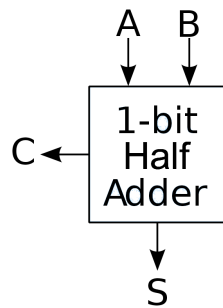

Circuit Diagram


Dimensions

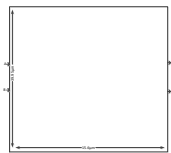

AC Characteristics

Signal		Delay (ps)
A to S/Cout prop delay (tPA)	256.2ps	B to S/Cout prop delay (tPB) 242.8ps

System Verilog Simulation

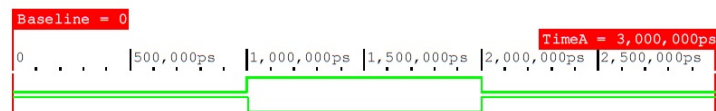


5 Inverter


Designer: Henry Lovett

Cell Description: A basic inverter gate

Symbol

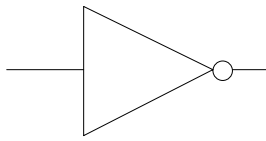


Dimensions

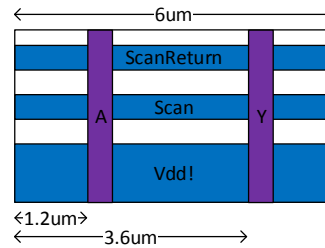

AC Characteristics

Signal	Delay (ps)
TO BE	DONE


System Verilog Simulation

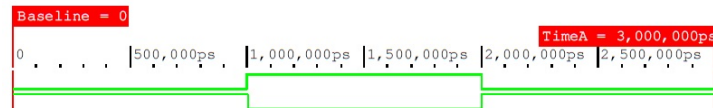

6 leftbuf

Designer: Henry Lovett
Cell Description: A start of row buffer cell.


Symbol Circuit Diagram Dimensions

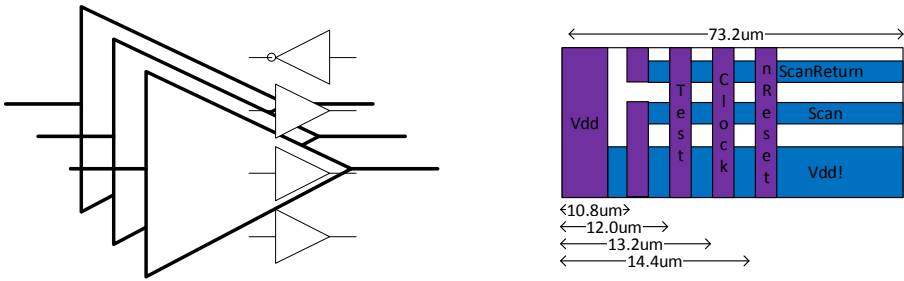

AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

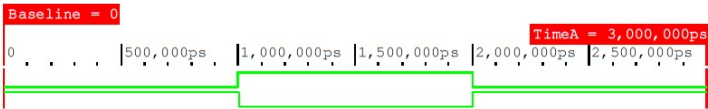


7 mux2


Designer: Constantijn Schepens

Cell Description: A two input Multiplexor

Symbol

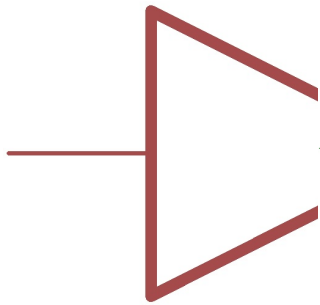

Circuit Diagram

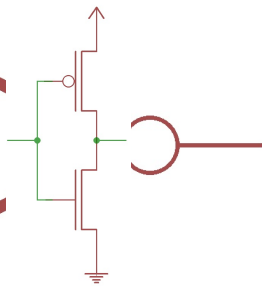


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

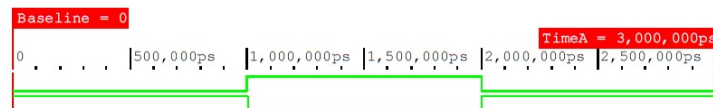


8 nand2


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

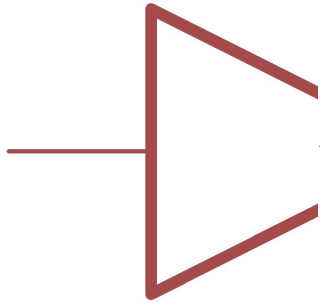

Circuit Diagram

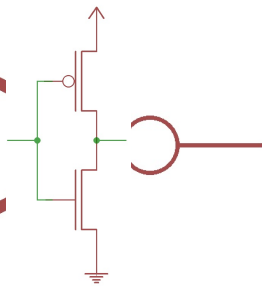


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

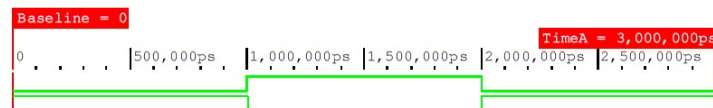


9 nand3


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

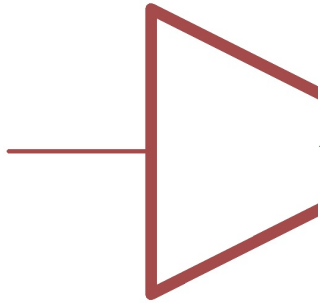

Circuit Diagram

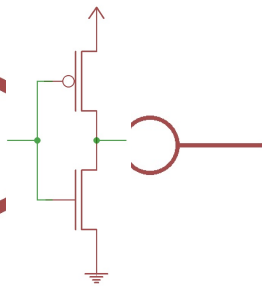


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

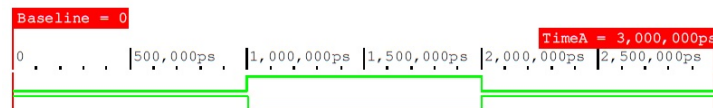


10 nand4


Designer: Constantijn Schepens

Cell Description: A two input NAND gate

Symbol

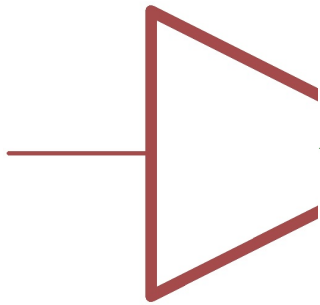

Circuit Diagram

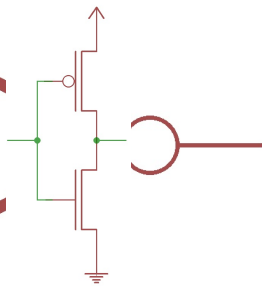


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

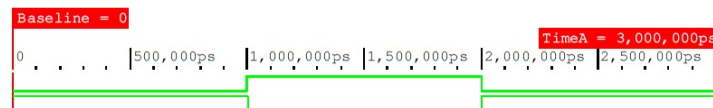


11 nor2


Designer: Henry Lovett

Cell Description: A two input NOR gate

Symbol

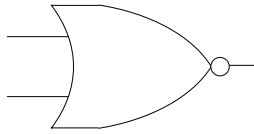


Dimensions

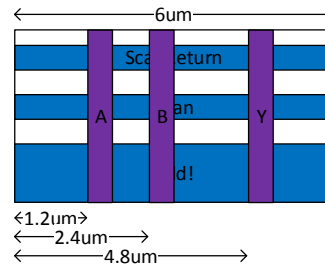

AC Characteristics

Signal	Delay (ps)
TO BE	DONE


System Verilog Simulation

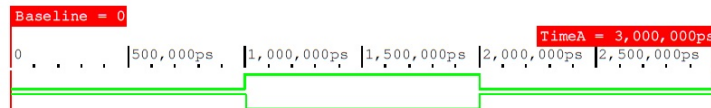


12 nor3

Designer: Henry Lovett
Cell Description: A three input NOR gate

Symbol

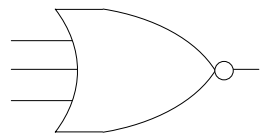


Dimensions

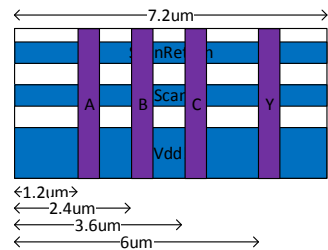

AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

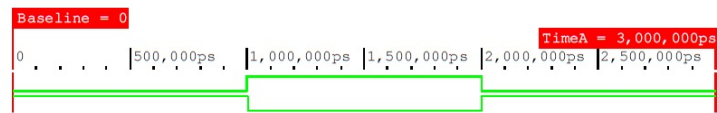


13 or2


Designer: Henry Lovett

Cell Description: A two input OR gate

Symbol

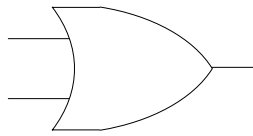


Dimensions

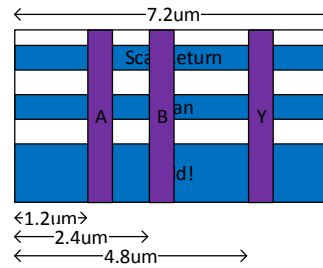

AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

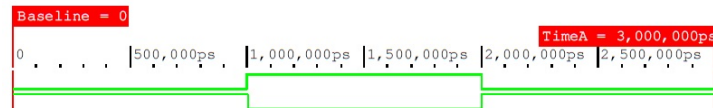


14 rightend


Designer: Henry Lovett

Cell Description: An end of row buffer cell.

Symbol

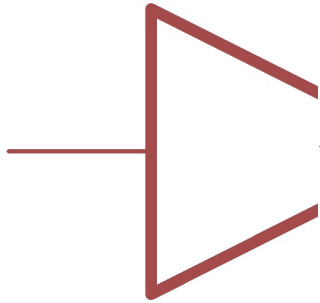

Circuit Diagram

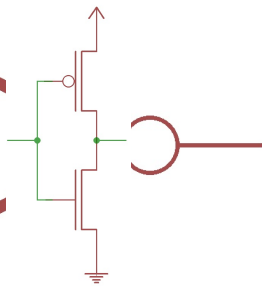


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

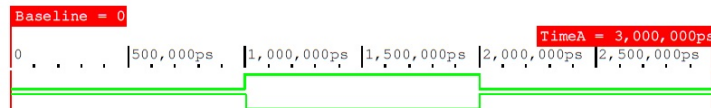

15 rowcrosser

Designer: Martin Wearn


Cell Description: A rowcrossing cell

16 scandtype


Designer: Constantijn Schepens

Cell Description: A Raw DType cell

Symbol

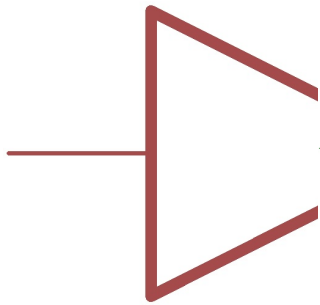

Circuit Diagram

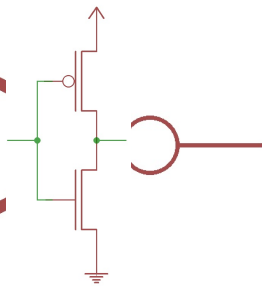


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

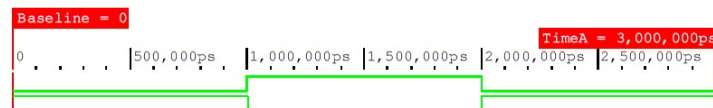


17 scanreg


Designer: Constantijn Schepens

Cell Description: A Raw DType cell

Symbol

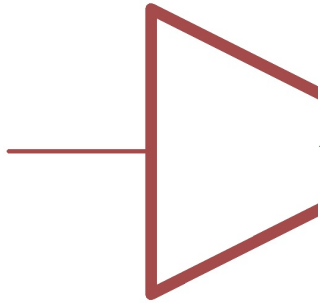

Circuit Diagram

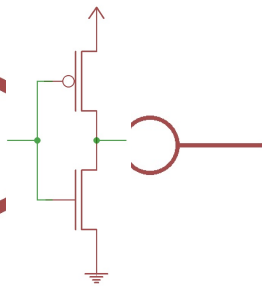


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

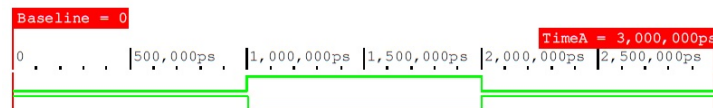

18 tiehigh

Designer: Martin Wearn

Cell Description: A tie to Vdd cell

19 tielow

Designer: Martin Wearn


Cell Description: A tie to GND cell

20 trisbuf


Designer: Ashley Robinson

Cell Description: A tristate buffer

Symbol

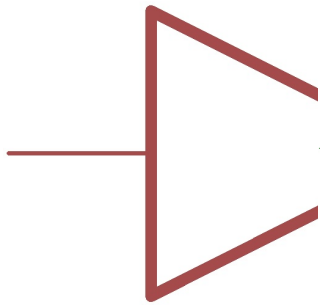

Circuit Diagram

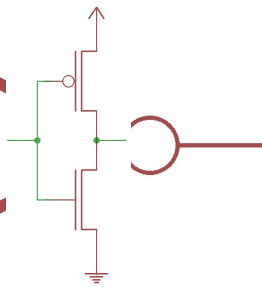


Dimensions



AC Characteristics

Signal	Delay (ps)
TO BE	DONE

System Verilog Simulation

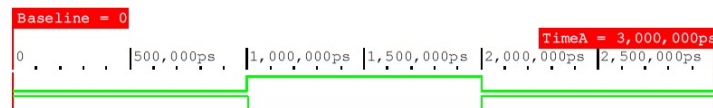


21 xor2


Designer: Ashley Robinson

Cell Description: A two input xor gate

Symbol

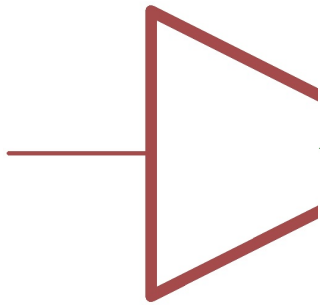

Circuit Diagram

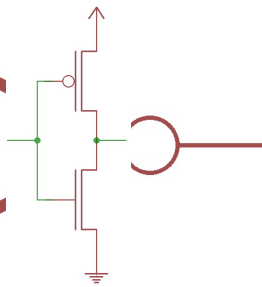


Dimensions



AC Characteristics

Signal	Delay (ps)
A to Y	273.4
B to Y	193

System Verilog Simulation

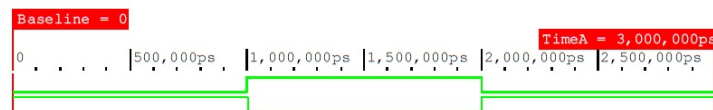

A Appendix A

A.1 Team Management

A.2 Division of Labour


B Design Detail

B.1 fulladder


Designer: Martin Wearn

Cell Description: Adds two bit values and the previous bitslice carry out, to produce a sum and carry

Stick Diagram

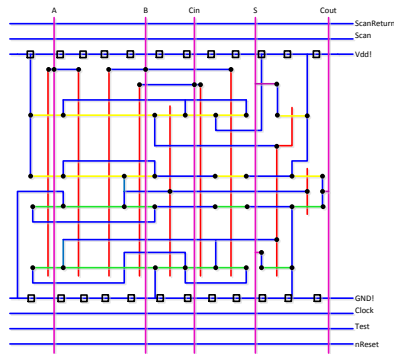

Transistor Level Circuit Diagram

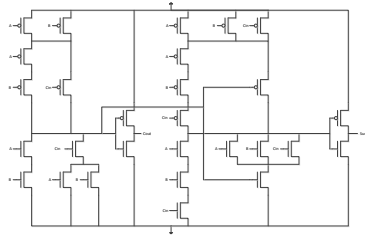


B.2 halfadder


Designer: Martin Wearn

Cell Description: Adds two bits to produce a sum and carry

Stick Diagram

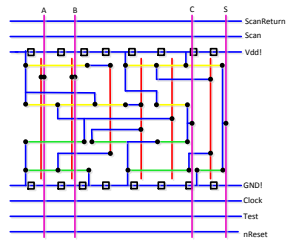

Transistor Level Circuit Diagram

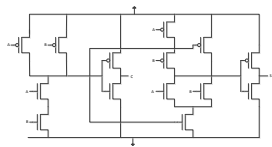


B.3 leftbuf


Designer: Henry Lovett

Cell Description: A start of row buffer cell.

Stick Diagram

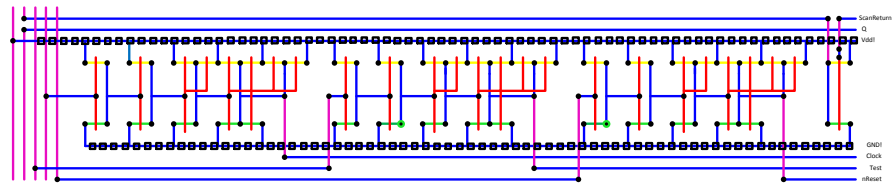

Transistor Level Circuit Diagram

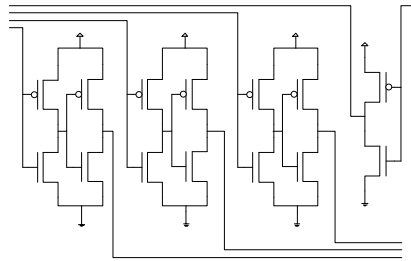


B.4 rdtype


Designer: Ashley Robinson

Cell Description: Raw Dtype

Stick Diagram

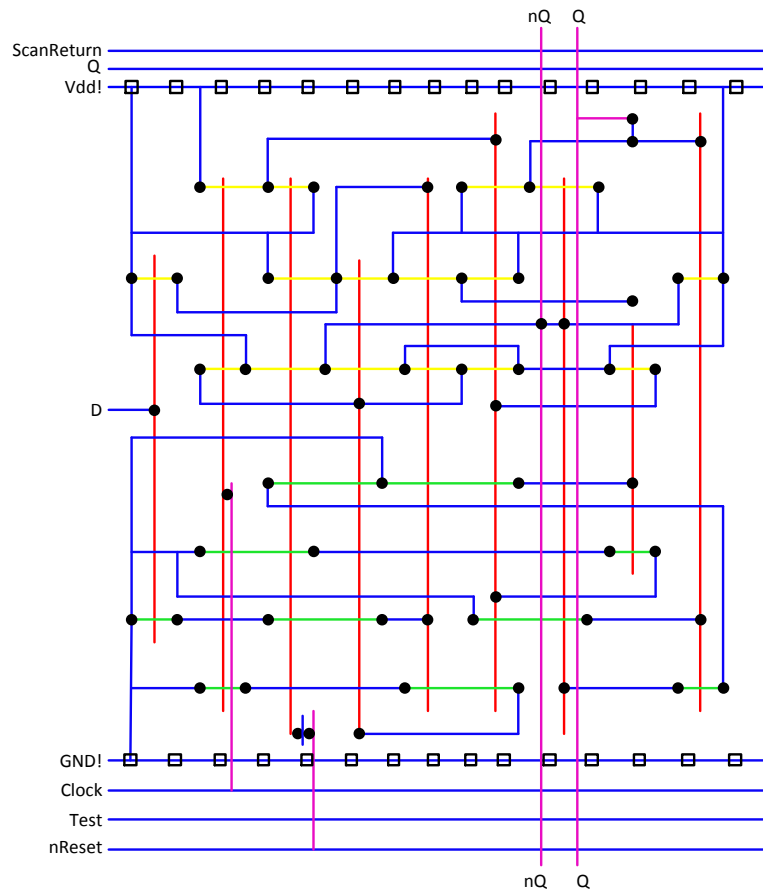

Transistor Level Circuit Diagram

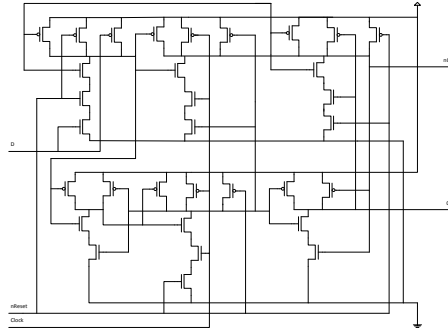


B.5 smux2


Designer: Schep

Cell Description: A start of row buffer cell.

Stick Diagram

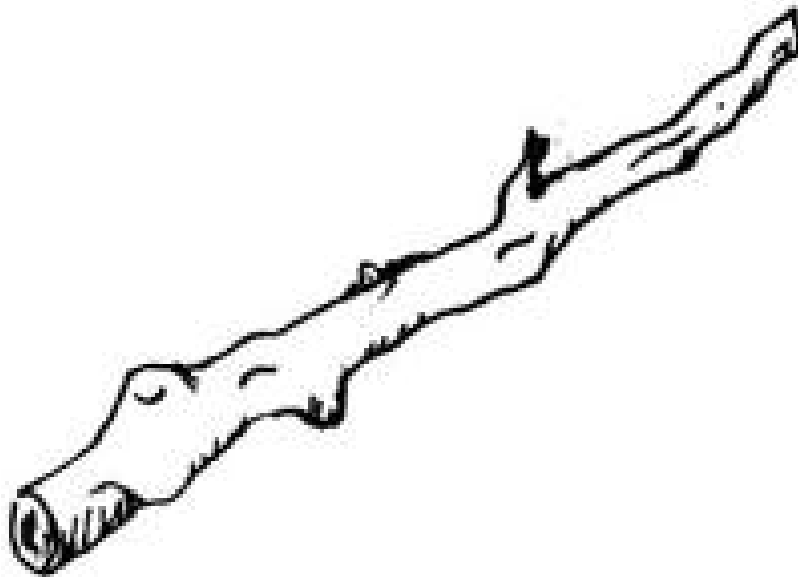

Transistor Level Circuit Diagram

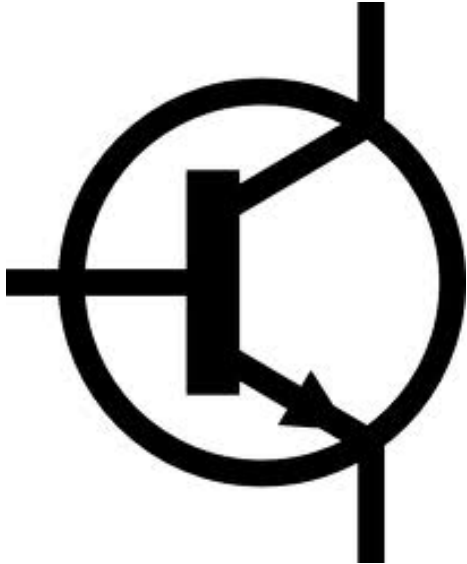


B.6 smux3


Designer: Schep

Cell Description: A scan multiplexor.

Stick Diagram

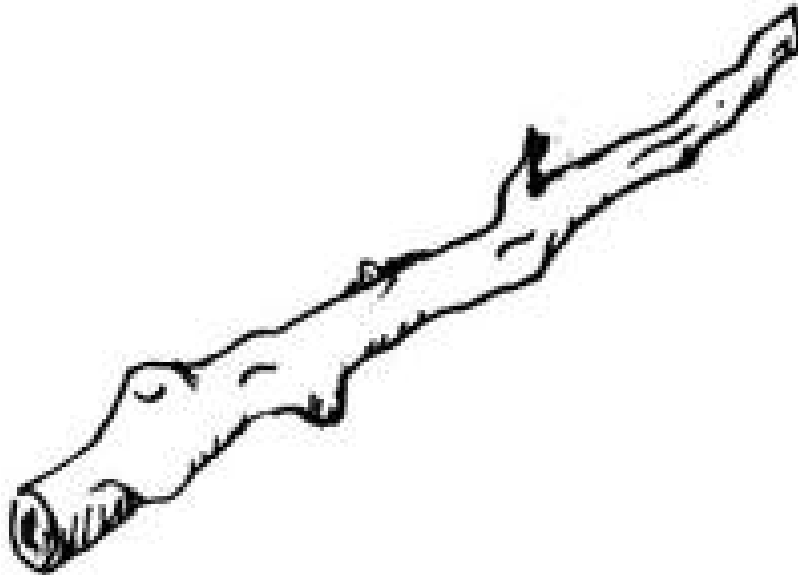

Transistor Level Circuit Diagram

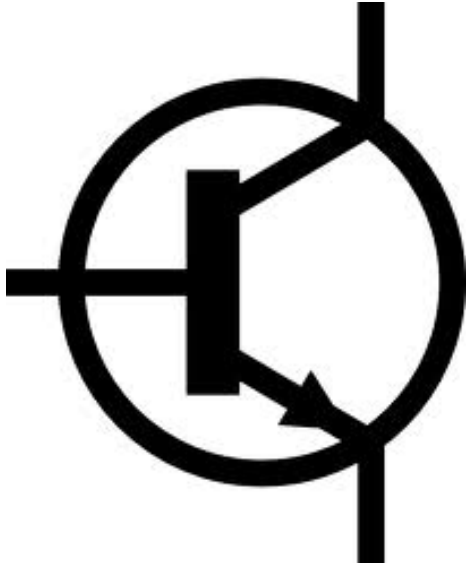


B.7 xor2

Designer: Ashley Robinson

Cell Description: A 2 input XOR gate.

Stick Diagram

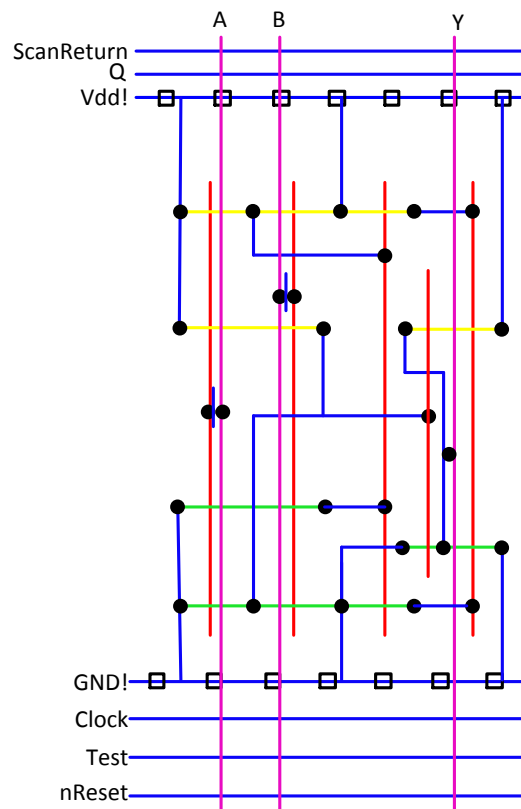

Transistor Level Circuit Diagram

